

## **6. Cascode Amplifiers and Cascode Current Mirrors**


Sedra & Smith Sec. 7 (MOS portion)

(S&S 5<sup>th</sup> Ed: Sec. 6 MOS portion & ignore frequency  
response)



# Cascode amplifier

## is a popular building block of ICs

### Cascode Configuration

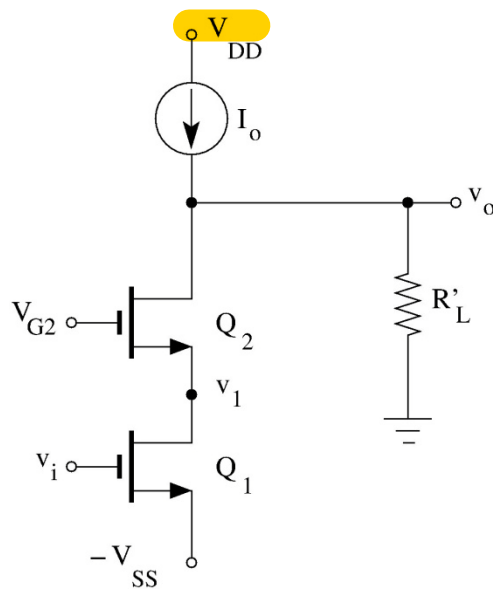


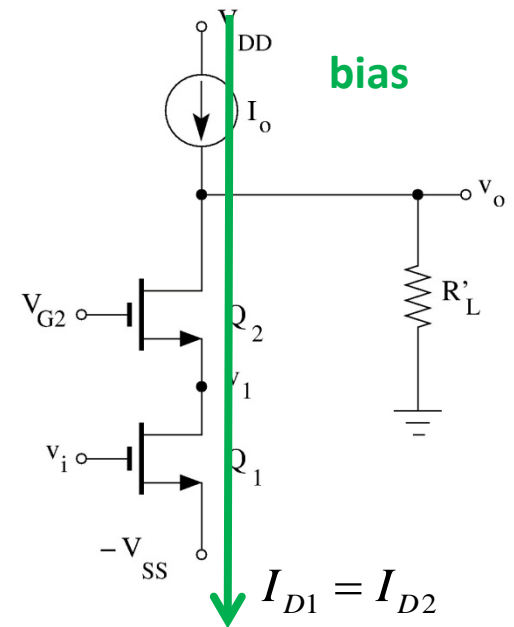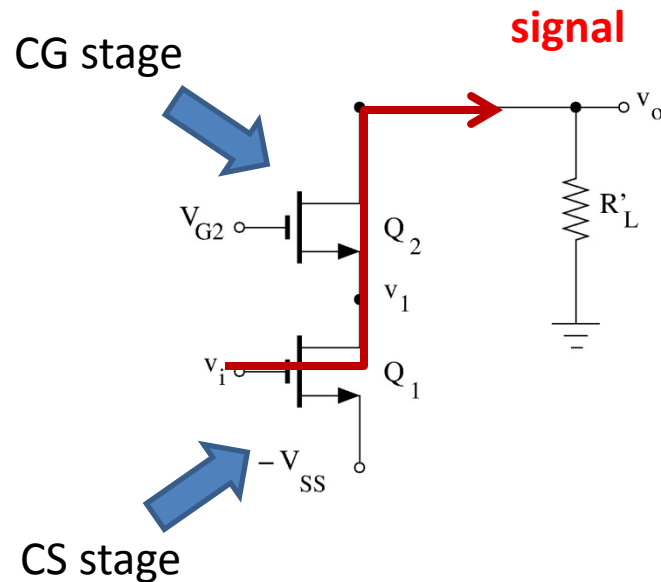Signal circuit: Current source becomes an open circuit




Cascode amplifier is a **two-stage, CS-CG configuration**
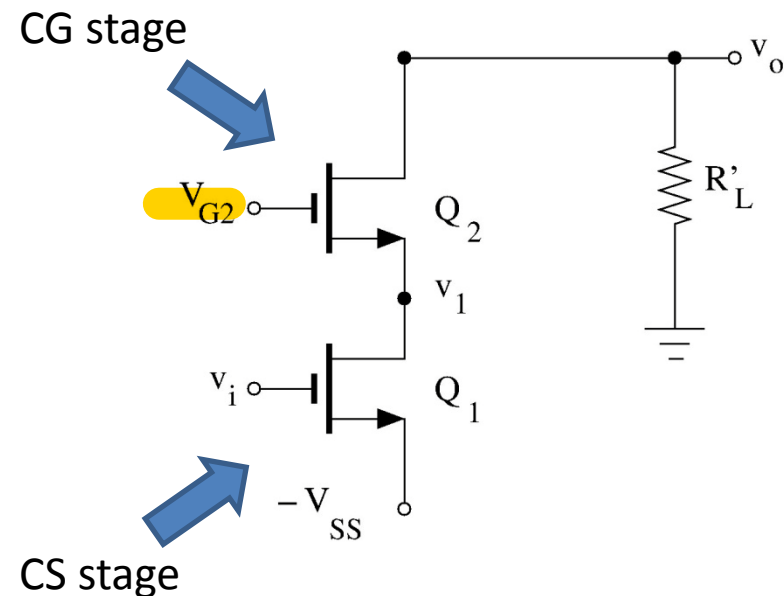
# Small Signal Model of a Cascode Amplifier




Small Signal Model

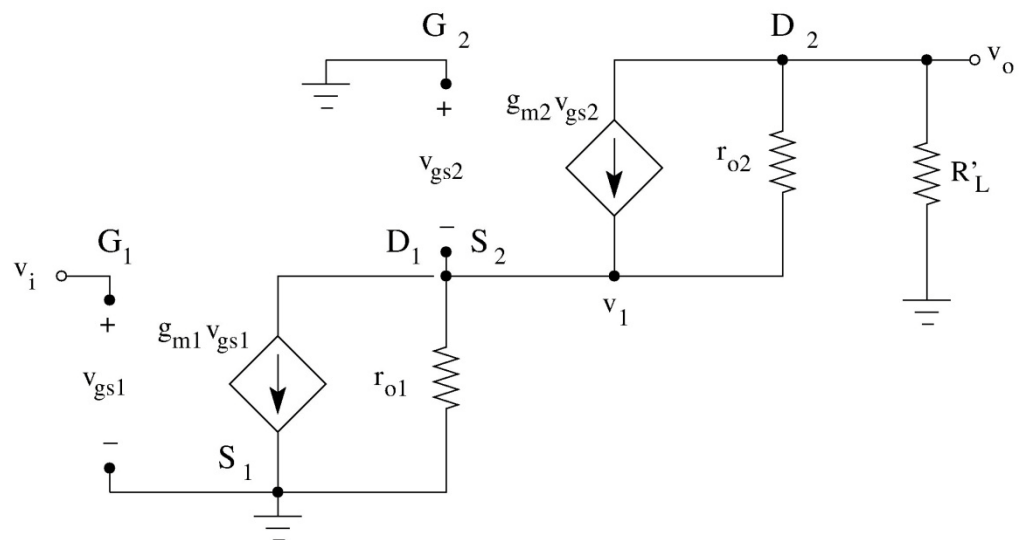

- Lengthy analysis to find  $A_v$  (and a complicated equation). **Simpler to compute open-loop gain ( $A_{vo}$ ) and  $R_o$ .**
- Text book introduces  $G_m$  method to find  $A_{vo}$  (See S&S Sec. 1)
- Here will find  $A_{vo}$  directly from the small signal model.
- **However, the solution of and insight into Cascode amplifiers are best obtained using fundamental MOS configurations!**

Note that  $A_{vo}$  and  $R_o$  calculated here are meant to find  $A_v$  and guide the choice of the active load.  $A_{vo}$  and  $R_o$  should be re-calculated for a practical circuit (see slides 14 & 15)
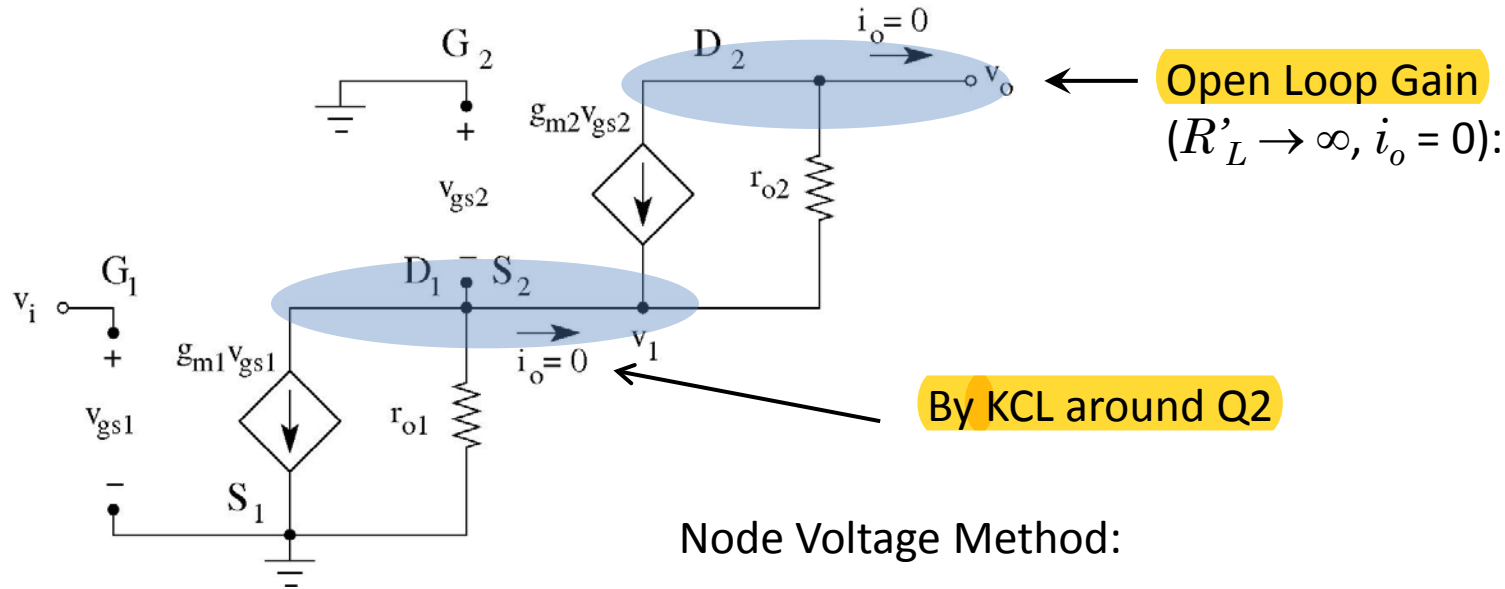
# Open-Loop gain of a Cascode amplifier (using small signal model)



Node Voltage Method:


$$\text{Node } v_o: \quad \frac{v_o - v_1}{r_{o2}} - g_{m2}v_1 = 0 \quad \Rightarrow \quad v_o = (1 + g_{m2}r_{o2})v_1$$

$$\text{Node } v_1: \quad \frac{v_1}{r_{o1}} + g_{m1}v_i + 0 = 0 \quad \Rightarrow \quad v_1 = -g_{m1}r_{o1}v_i$$


$$A_{vo} = \frac{v_o}{v_i} = -g_{m1}r_{o1} \times (1 + g_{m2}r_{o2}) \approx -g_{m1}r_{o1}g_{m2}r_{o2}$$
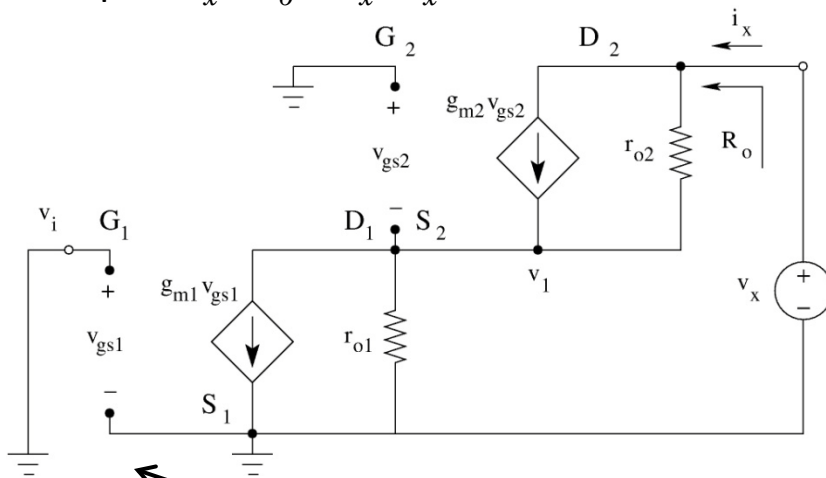
# Output Resistance of a Cascode amplifier (using small signal model)

Set  $v_i = 0$ , attach a voltage source  $v_x$ ,  
compute  $i_x$ ,  $R_o = v_x / i_x$



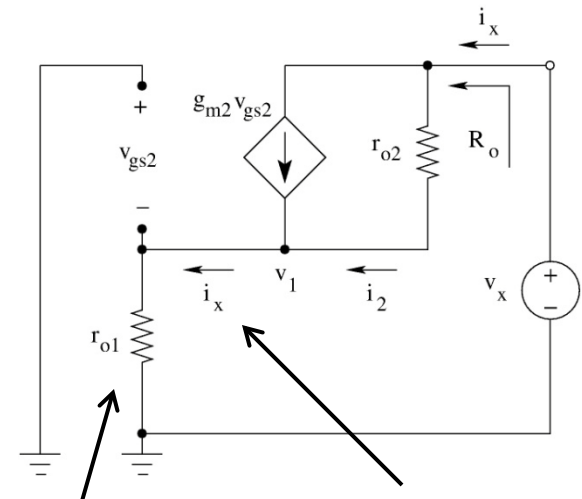$v_i = v_{gs1} = 0 \rightarrow g_{m1} v_{gs1}$  current source becomes open circuit



By KCL around Q2

$$\text{KVL : } v_{gs2} = -i_x r_{o1}$$

$$\text{KCL : } i_2 = i_x - g_{m2} v_{gs2} = i_x + i_x g_{m2} r_{o1} = i_x (1 + g_{m2} r_{o1})$$

$$\text{KVL : } v_x = i_2 r_{o2} + i_x r_{o1} = i_x (1 + g_{m2} r_{o1}) r_{o2} + i_x r_{o1}$$


$$v_x = i_x [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$$

$$R_o = \frac{v_x}{i_x} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}$$


Note:  $A_v = A_{vo} \times \frac{R'_L + R_o}{R'_L}$

# Gain of a Cascode Amplifier (using MOS Fundamental Configurations)


Cascode (signal circuit)

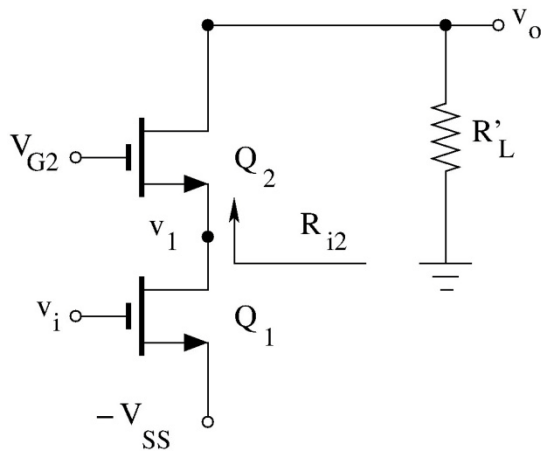

CG stage

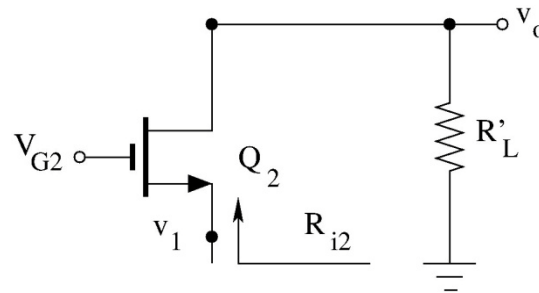

CS stage

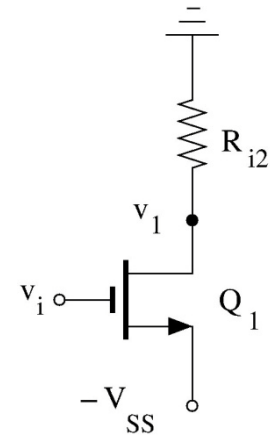

$$A_{v2} = v_o / v_1 \approx g_{m2} (r_{o2} \parallel R'_L)$$

$$A_{v1} = v_1 / v_i = -g_{m1} (r_{o1} \parallel R_{i2})$$


CG stages "reduces" the load  
seen by the CS stage by  $g_{m2}r_{o2}$

$$R_{L1} = R_{i2} = \frac{r_{o2} + R'_L}{1 + g_{m2}r_{o2}}$$

$$A_v = v_o / v_i = A_{v1} A_{v2} = -g_{m1} g_{m2} (r_{o1} \parallel R_{i2}) (r_{o2} \parallel R'_L)$$

**Note:** Open Loop Gain:  $(R'_L \rightarrow \infty)$   $R_{L1} = R_{i2} = \frac{r_{o2} + R'_L}{1 + g_{m2}r_{o2}} = \infty \rightarrow A_{vo} = -g_{m1}r_{o1}g_{m2}r_{o2}$
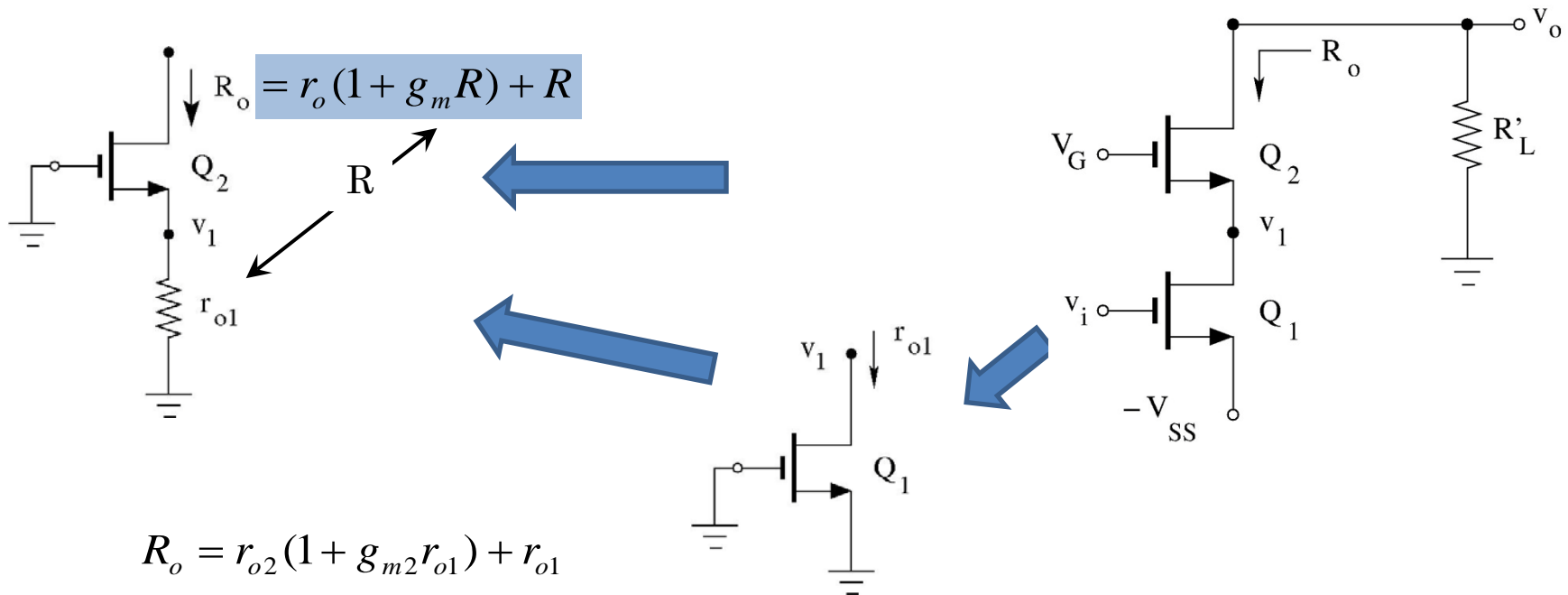
# Output Resistance of a Cascode amplifier (from Elementary R forms)



$$R_o = r_{o2}(1 + g_{m2}r_{o1}) + r_{o1}$$

$$R_o = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}$$

$$R_o = r_{o2}(1 + g_{m2}r_{o1}) + r_{o1}$$

$$R_o \approx g_{m2}r_{o2}r_{o1} + r_{o1} = r_{o1}(1 + g_{m2}r_{o2})$$

$$R_o \approx g_{m2} r_{o1} r_{o2}$$

# Cascode Amplifier needs a large load

$$A_{v2} = g_{m2}(r_{o2} \parallel R'_L)$$

$$R_{L1} = R_{i2} = \frac{r_{o2} + R'_L}{1 + g_{m2}r_{o2}}$$

$$A_{v1} = -g_{m1}(r_{o1} \parallel R_{i2})$$

$$R_o \approx g_{m2} r_{o1} r_{o2}$$


For simplicity assume  $r_{o1} = r_{o2} = r_o$  and  $g_{m1} = g_{m2} = g_m$

$R'_L$	$A_{v2}(\text{CG})$	$R_{i2} = R_{L1}$	$A_{v1}(\text{CS})$	$A_v = A_{v1} A_{v2}$	
$\infty$	$g_m r_o$	$\infty$	$-g_m r_o$	$-(g_m r_o)^2$	Max. Gain
$(g_m r_o) r_o = R_o$	$g_m r_o$	$r_o$	$-0.5 g_m r_o$	$-0.5 (g_m r_o)^2$	Practical Gain
$r_o$	$0.5 g_m r_o$	$2/g_m$	$-2$	$-g_m r_o$	Same gain as a single CS Amp.

- For comparison, a two-stage CS-amplifier (CS-CS) has a gain of  $0.5 (g_m r_o)^2$  for  $R'_L = r_o$  and a gain of  $(g_m r_o)^2$  for  $R'_L = g_m r_o^2$ .
  - Cascode amplifier needs a large load ( $R'_L = g_m r_o^2$ ).


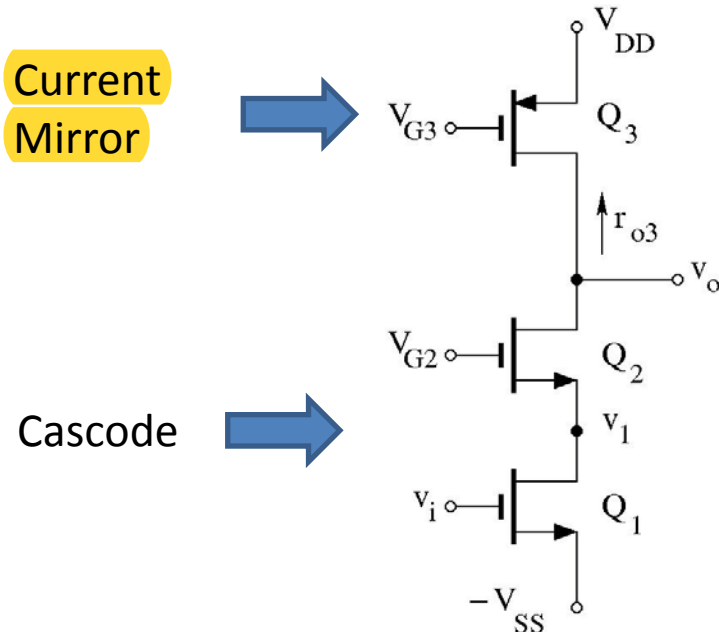
# Cascode amplifier needs a large load to get a high gain




$$R'_L = r_{o3}$$

$$A_v \approx -g_m r_o$$

- Gain did not increase compared to a CS amplifier.
- This is still a useful circuit because of its high gain-bandwidth (we see this later).
- To get a high gain,  $A_v = -0.5(g_m r_o)^2$ , we need to increase the small-signal resistance of the current mirror to  $\approx (g_m r_o) r_o$ 
  - Cascode current mirror

# Cascode Current mirror

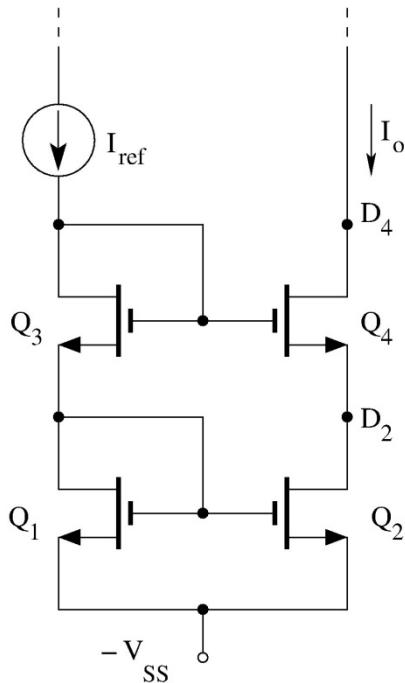





- Identical MOS: Same  $\mu C_{ox}$  and  $V_t$ , &  $\frac{(W/L)_4}{(W/L)_3} = \frac{(W/L)_2}{(W/L)_1}$ 
  - $v_{GS1} = v_{GS2}$  &  $v_{GS3} = v_{GS4}$
- Usually:  $(W/L)_1 = (W/L)_3$  and  $(W/L)_2 = (W/L)_4$ 
  - $v_{GS1} = v_{GS2} = v_{GS3} = v_{GS4} = v_{GS}$

- Q1 and Q3 are always in **saturation**
- Q2 and Q4 both have to be in saturation for **current mirror to work**
  - $V_{DS2} > V_{GS} - V_t$
  - $V_{DS4} > V_{GS} - V_t$
- **Straight forward to** show  $I_o = \frac{(W/L)_2}{(W/L)_1} I_{ref}$

**Exercise:** Show that a **single current mirror** (no cascoding) works only if  $V_{D2} > V_{OV} - V_{SS}$  and a cascode current mirror requires  $V_{D4} > 2V_{OV} - V_{SS}$
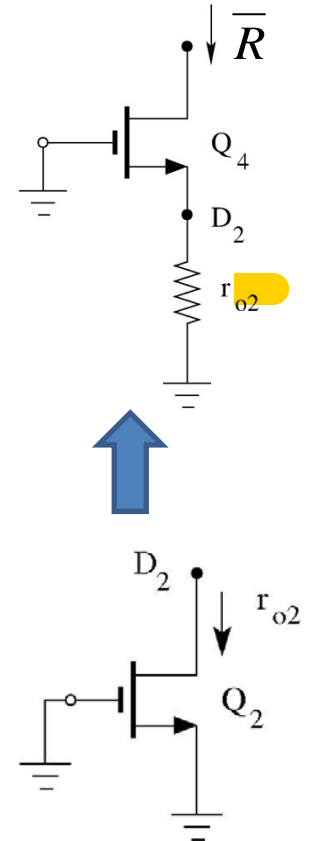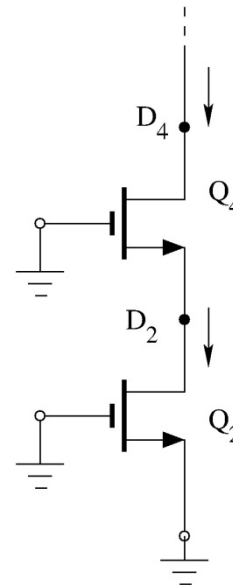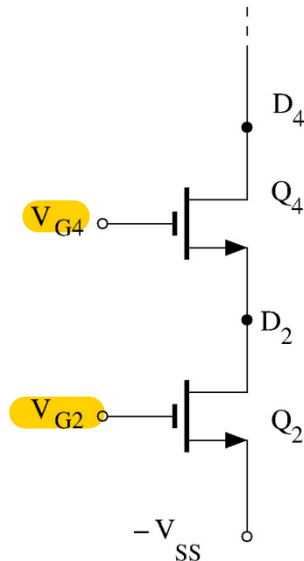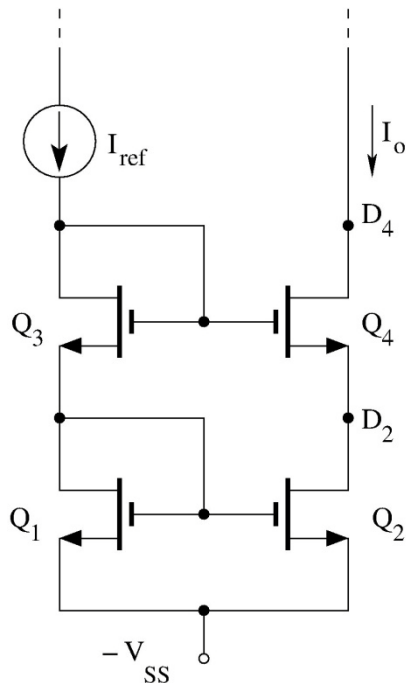
# Small signal resistance of a cascode current mirror is quite large

$$\bar{R} = r_{o4}(1 + g_{m4}r_{o2}) + r_{o2}$$




Transistor numbering is different in different circuits

Be careful in applying formulas!


It is best to use elementary R forms to find  $\bar{R}$  instead of formula above.

# PMOS cascode current mirror is similar to NMOS version


NMOS **Cascode current mirror**

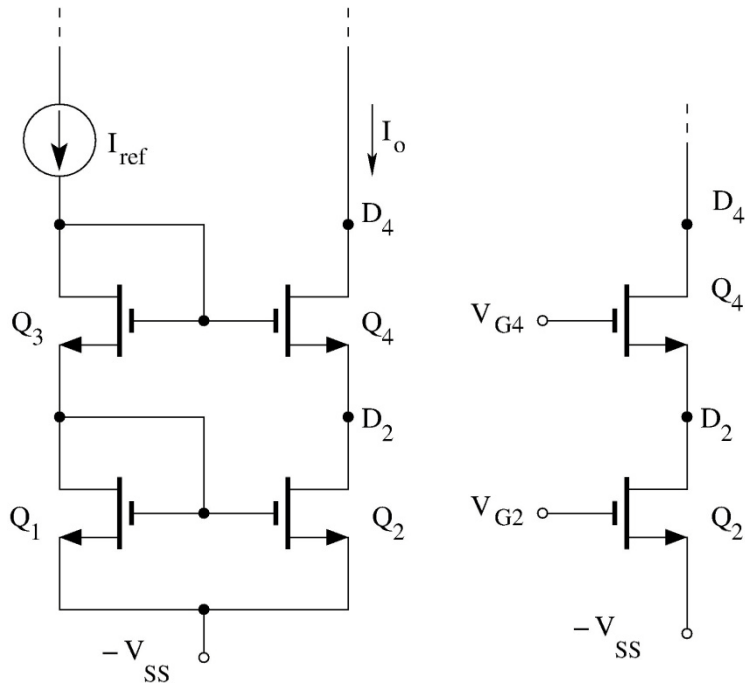

PMOS Cascode current mirror


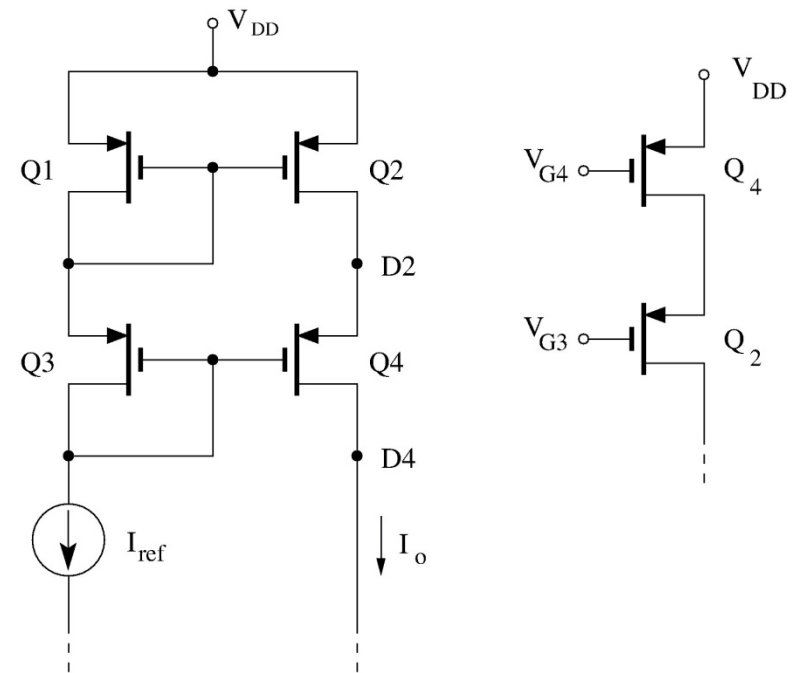

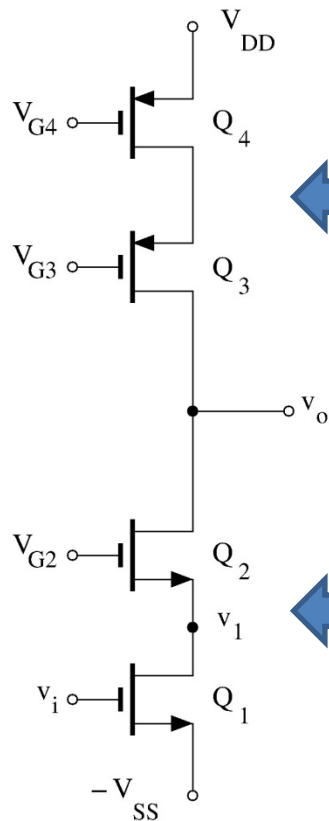
# Cascode amplifier with a cascode current mirror/active load



Cascode  
current mirror


Cascode  
amplifier

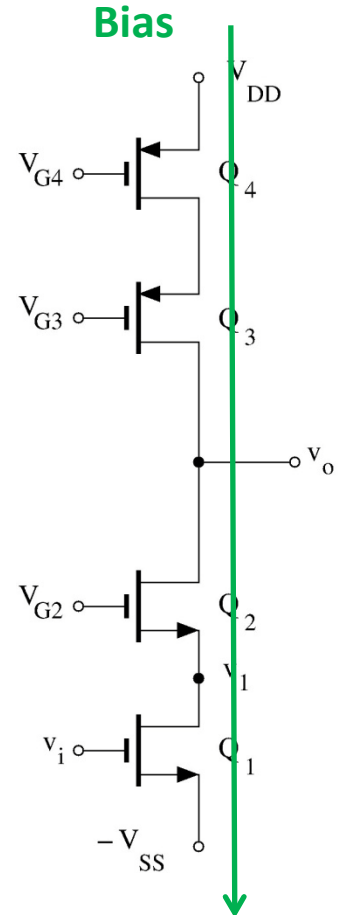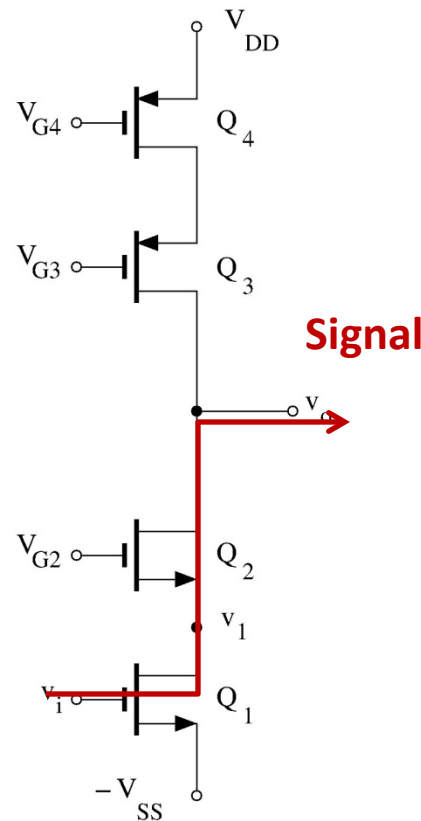

$$I_{D1} = I_{D2} = I_{D3} = I_{D4}$$

Exercise: Draw the circuit for a PMOS cascode with a cascode current mirror (cascode current mirror would be made of NMOS).
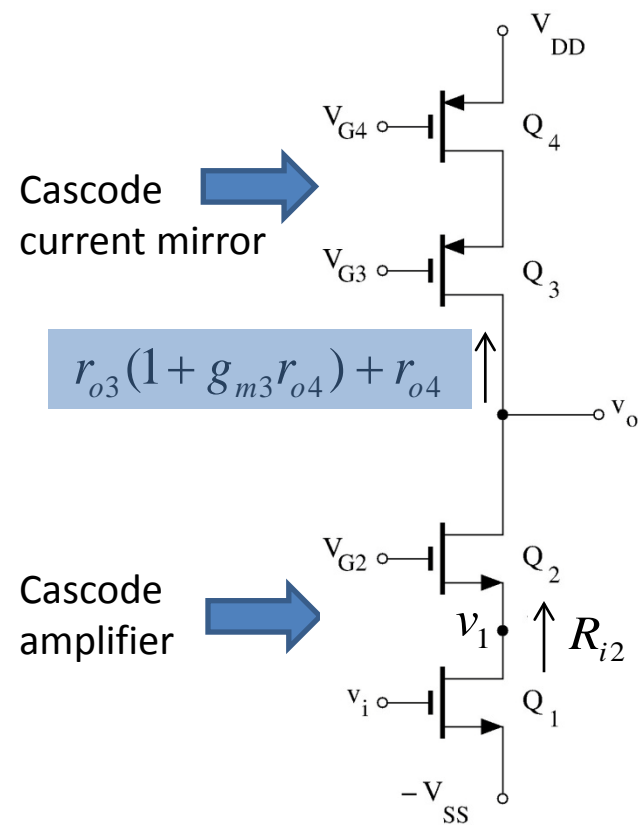
# Gain of a Cascode amplifier with a cascode current mirror/active load



## Q2 (CG Amp)

$$A_{v2} = v_o / v_1 \approx g_{m2}(r_{o2} \parallel R'_L) \approx g_{m2}r_{o2}$$

$$R_{L1} = R_{i2} = \frac{r_{o2} + r_{o3}(1 + g_{m3}r_{o4}) + r_{o4}}{1 + g_{m2}r_{o2}} \approx \frac{g_{m3}r_{o3}r_{o4}}{g_{m2}r_{o2}}$$

## Q1 (CS Amp)

$$A_{v1} = v_1 / v_i = -g_{m1}(r_{o1} \parallel \frac{g_{m3}r_{o3}r_{o4}}{g_{m2}r_{o2}})$$

$$A_{vo} = A_{v1}A_{v2} = -\frac{g_{m1}g_{m2}g_{m3}r_{o1}r_{o2}r_{o3}r_{o4}}{g_{m2}r_{o1}r_{o2} + g_{m3}r_{o3}r_{o4}}$$

## Value for the same

$g_m$  and  $r_o$


$$A_{v2} \approx g_m r_o$$

$$R_{L1} = R_{i2} \approx r_o$$

$$A_{v1} = -0.5 g_m r_o$$

$$A_{vo} = -0.5 (g_m r_o)^2$$
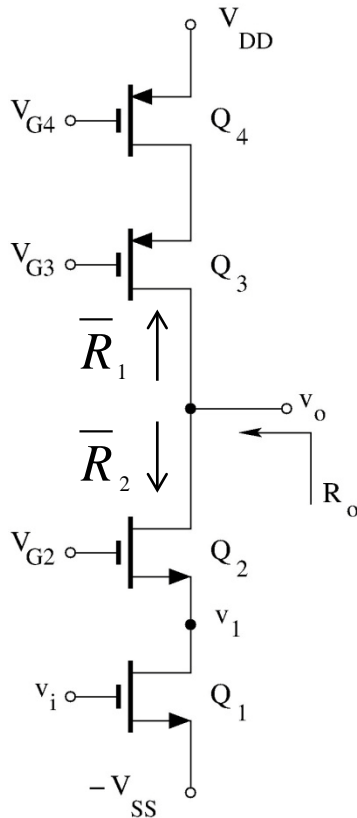
# Output Resistance of a Cascode amplifier with a cascode current mirror/active load



$$\bar{R}_1 = r_{o3}(1 + g_{m3}r_{o4}) + r_{o4}$$

$$\bar{R}_2 = r_{o2}(1 + g_{m2}r_{o1}) + r_{o1}$$

$$R_o = \bar{R}_1 \parallel \bar{R}_2$$

Value for the same  $g_m$  and  $r_o$

$$\bar{R}_1 \approx g_m r_o^2$$

$$\bar{R}_2 \approx g_m r_o^2$$


$$R_o \approx 0.5 g_m r_o^2$$

# Why Cascode Amplifiers are popular?

## Cascode Amp.

$$A_{vo} = -0.5 (g_m r_o)^2$$

$$R_o = 0.5 g_m r_o^2$$

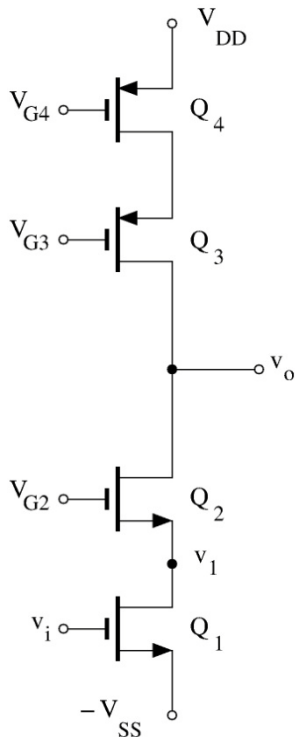

### Drawbacks:

- While  $A_{vo}$  are similar, Cascode has a very  $R_o$  (M $\Omega$  level).
  - should be followed with a CS or CD stage (infinite load for cascode)
  - BJT cascodes are not useful.
- Low voltage headroom ( $V_{DD}$  across 4 MOS)
  - Folded cascodes solve this.


### Benefits:

- Much better high-frequency response (high gain-bandwidth).\*
- Simpler biasing.

## 2-stage CS Amp.

$$A_{vo} = +0.25 (g_m r_o)^2$$


$$R_o = r_o$$

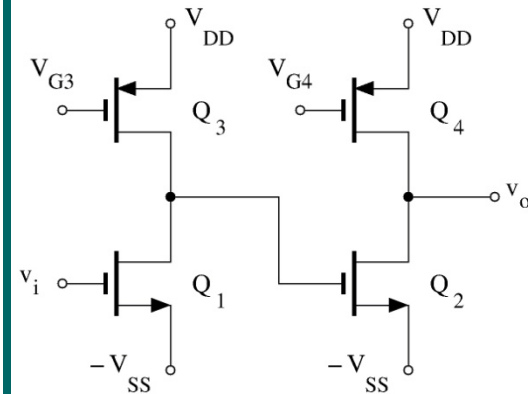

\* We will see this later in our discussion of frequency response.


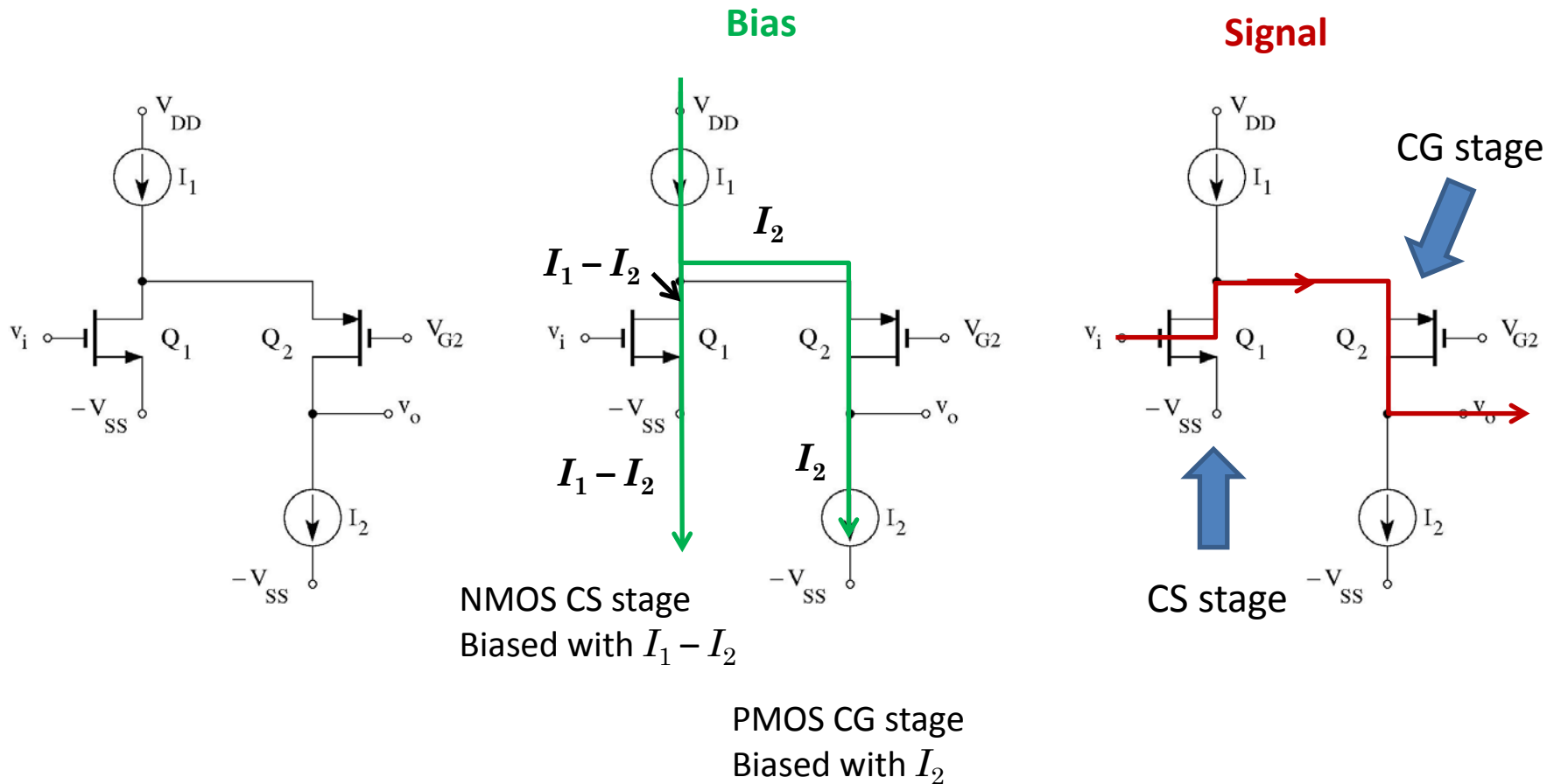
# Folded Cascode increases voltage overhead\*



\* Folded cascode only helps the voltage overhead issue for difference amplifiers (see S&S pages 999-1000)