

Exercises for MOS Device Operation and Large Signal Model


Exercise 1: Compute i_D and v_{DS} in the circuit below. MOS has $V_{t,n} = 0.4$ V and $\mu_n C_{ox} (W/L) = 1.0$ mA/V² for A) Ignoring Channel-Width Modulation, b) Including channel-width modulation with $\lambda = 0.05$ V⁻¹.

➤ It is generally advantageous to solve for $V_{OV} = V_{GS} - V_t$ (instead of V_{GS}).

$$i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2 [1 + \lambda v_{DS}]$$

➤ Ignoring channel width modulation introduces a relative error in circuit parameters (e.g., i_D) of $\sim \lambda v_{DS}$.

 - This is an acceptable error in most biasing calculations.



$$V_{OV} = v_{GS} - V_{t,n} = v_G - v_S - V_{t,n} = 1 - 0 - 0.4 = 0.6 \text{ V}$$


Assume Saturation*: $V_{OV} \geq 0$ and $v_{DS} \geq V_{OV}$

A) $\lambda = 0$

$$\text{Saturation : } i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2 = 0.5 \times 1.0 \times 10^{-3} \times (0.6)^2 = 0.180 \text{ mA}$$

$$\text{KVL : } 1.8 = 5 \times 10^3 i_D + v_{DS} \Rightarrow v_{DS} = 1.8 - 5 \times 10^3 \times (0.18 \times 10^{-3}) = 0.90 \text{ V}$$

 (Expected error in i_D and v_{DS} is $\sim \lambda v_{DS} = 0.05 \times 0.90 = 4.5\%$)



B) $\lambda = 0.05 \text{ V}^{-1}$

$$\text{Saturation : } i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2 [1 + \lambda v_{DS}] = 0.18 \times 10^{-3} [1 + 0.05 v_{DS}]$$

$$\text{KVL : } 1.8 = 5 \times 10^3 i_D + v_{DS} \Rightarrow 1.8 = 5 \times 10^3 \times (0.18 \times 10^{-3}) (1 + 0.05 v_{DS}) + v_{DS}$$

$$1.8 = 0.9 + 0.045 v_{DS} + v_{DS} \Rightarrow v_{DS} = 0.86 \text{ V}$$

$$i_D = 0.18 \times 10^{-3} [1 + 0.05 v_{DS}] = 0.188 \text{ mA}$$

*Note $V_{OV} \geq 0$ and $v_{DS} \geq V_{OV}$ for both cases, so assumption of saturation is justified.

Exercise 2: An NMOS $\mu_n C_{ox} (W/L) = 0.1 \text{ mA/V}^2$ and $V_t = 0.5 \text{ V}$ is to be operated in the saturation region. If $i_D = 12.5 \text{ } \mu\text{A}$, find the required v_{GS} and the minimum required v_{DS} . Ignore channel width modulation.

$$\text{Saturation : } V_{OV} \geq 0 \text{ and } v_{DS} \geq V_{OV} \qquad i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2 [1 + \lambda v_{DS}]$$

$$\lambda = 0 \Rightarrow i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$

$$12.5 \times 10^{-6} = 0.5 (0.1 \times 10^{-3}) V_{OV}^2$$

$$V_{OV} = 0.5 \text{ V}$$

$$v_{GS} = V_{OV} + V_t = 1 \text{ V}$$

$$\text{For NMOS in saturation : } v_{DS} \geq V_{OV} = 0.5 \text{ V} \Rightarrow \text{Minimum } v_{DS} = 0.5 \text{ V}$$

An important aspect of amplifier design is to ensure that MOS is always in saturation.

Exercise 3: The PMOS transistor in the circuit below has $V_{t,p} = -0.5$ V. As the gate voltage, v_G , is varied from +2.5 V to 0, PMOS moves through all of its three states. Find values of v_G at which the device changes modes of operation.

$$v_{SD} = v_S - v_D = 2.5 - 1 = 1.5 \text{ V}$$

$$V_{OV} = v_{SG} - |V_{t,p}| = v_S - v_G - |V_{t,p}| = 2.5 - v_G - 0.5 = 2.0 - v_G$$


Cut - Off : $V_{OV} \leq 0 \Rightarrow 2.0 - v_G \leq 0 \Rightarrow v_G \geq 2.0 \text{ V}$

Triode : $V_{OV} \geq 0 \Rightarrow v_G \leq 2.0 \text{ V}$

and $v_{SD} \leq V_{OV} \Rightarrow 1.5 \leq V_{OV} = 2.0 - v_G \Rightarrow v_G \leq 2.0 - 1.5 = 0.5 \text{ V}$

Saturation : $V_{OV} \geq 0 \Rightarrow v_G \leq 2.0 \text{ V}$

 and $v_{SD} \geq V_{OV} \Rightarrow 1.5 \geq V_{OV} = 2.0 - v_G \Rightarrow v_G \geq 2.0 - 1.5 = 0.5 \text{ V}$



$$v_G \leq 0.5 \text{ V}$$

$$0.5 \leq v_G \leq 2 \text{ V}$$

Transition from cut-off to saturation at $v_G = 2 \text{ V}$
 transition from saturation to triode at $v_G = 0.5 \text{ V}$

Exercise 4: Find V_S for $\mu_p C_{ox} (W/L) = 0.5 \text{ mA/V}^2$, $V_{tp} = -0.6 \text{ V}$ and $\lambda = 0$).

- Since $i_D = 40 \text{ }\mu\text{A}$, PMOS is ON
- Assume PMOS in saturation

$$i_D = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$


$$40 \times 10^{-6} = 0.5 \times 0.5 \times 10^{-3} V_{OV}^2 \rightarrow V_{OV} = 0.4 \text{ V}$$

$$v_{SG} = V_{OV} + |V_{tp}| = 0.4 + 0.6 = 1 \text{ V}$$

$$v_{SG} = V_S - V_G = V_S - 0 \rightarrow \underline{V_S = 1 \text{ V}}$$

$$v_{SD} = V_S - V_D = 1 - (-5) = 6 \text{ V}$$

$$v_{SD} = 6 > V_{OV} = 0.4 \text{ V} \quad (\text{PMOS in saturation})$$

 

Exercise 5: Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and ignore channel-width modulation).

$$\text{GS1-KVL: } 0 = v_{GS1} + 10^3 i_D - 2.5 = V_{OV1} + V_t + 10^3 i_D - 2.5$$


$$\rightarrow V_{OV1} + 10^3 i_D = 1.5$$

$$\text{GS2-KVL: } 2.5 = v_{GS2} + v_{DS1} + 10^3 i_D - 2.5$$

$$\text{DS-KVL: } 2.5 = v_{DS2} + v_{DS1} + 10^3 i_D - 2.5$$

$$\text{KCL: } i_{D1} = i_{D2} = i_D$$

 - Q1 is not in cut-off since for $i_{D1} = 0$, GS1-KVL gives $V_{OV} = 1.5 \text{ V} > 0$.
 - Q2 is not in cut-off either as $i_{D2} = i_D > 0$



Exercise 5 (cont'd): Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and ignore channel-width modulation).

Assume both MOS in saturation

$$i_D = i_{D1} = 0.5 \mu_n C_{ox} \frac{W}{L} V_{OV1}^2$$

$$\text{GS1-KVL: } 1.5 = V_{OV1} + 10^3 i_D = V_{OV1} + 10^3 \times 0.5 \times 5 \times 10^{-3} V_{OV1}^2$$

$$2.5 V_{OV1}^2 + V_{OV1} - 1.5 = 0$$

$$V_{OV1} = -1.0 \text{ V} \quad (\text{incorrect, need } V_{OV} > 0)$$

$$V_{OV1} = 0.60 \text{ V}$$


Both MOS in saturation, $i_{D2} = i_{D1}$ and $\lambda = 0$: $V_{OV2} = V_{OV1} = 0.60 \text{ V}$

$$v_{GS1} = V_{OV1} + V_t = 0.6 + 1 = 1.6 \text{ V}$$

$$v_{GS1} = V_{G1} - V_{S1} = 0 - V_2 \rightarrow V_2 = -1.6 \text{ V}$$

$$v_{GS2} = V_{OV2} + V_t = 0.6 + 1 = 1.6 \text{ V}$$
 
$$v_{GS2} = V_{G2} - V_{S2} = 2.5 - V_1 \rightarrow V_1 = 0.9 \text{ V}$$



Exercise 5 (cont'd): Find V_1 and V_2 ($\mu_n C_{ox} (W/L) = 5 \text{ mA/V}^2$, $V_t = 1 \text{ V}$, and ignore channel-width modulation).


Need to confirm our assumption of both MOS in saturation

$$v_{DS1} = V_{D1} - V_{S1} = V_1 - V_2 = 0.90 - (-1.6) = 2.5 \text{ V}$$

$$v_{DS1} = 2.5 > V_{OV1} = 0.6 \text{ V}$$

$$v_{DS2} = V_{D2} - V_{S2} = 2.5 - V_1 = 2.5 - 0.9 = 1.6 \text{ V}$$
 
$$v_{DS2} = 1.6 > V_{OV2} = 0.6 \text{ V}$$



For circuits with multiple transistors, it is usually advantageous to keep track of node voltages (at transistor terminals!)