


2. Introduction to MOS Amplifiers: Concepts and MOS Small-Signal-Model

Sedra & Smith Sec. 5.4 & 5.6

(S&S 5th Ed: Sec. 4.4 & 4.6)

NMOS Transfer Function (1)

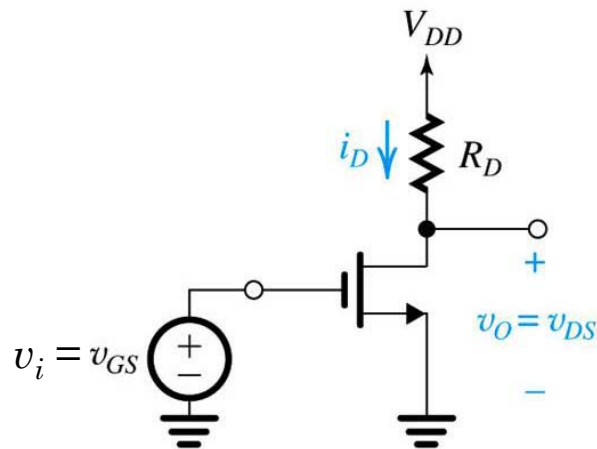- Transfer Function: Relation between output and input voltages.




Circuit Equations:

- NMOS i_v characteristics: $i_D = f(v_{GS}, v_{DS})$
- KVL: $v_o = v_{DS} = V_{DD} - R_D i_D$

NMOS Transfer Function (2)

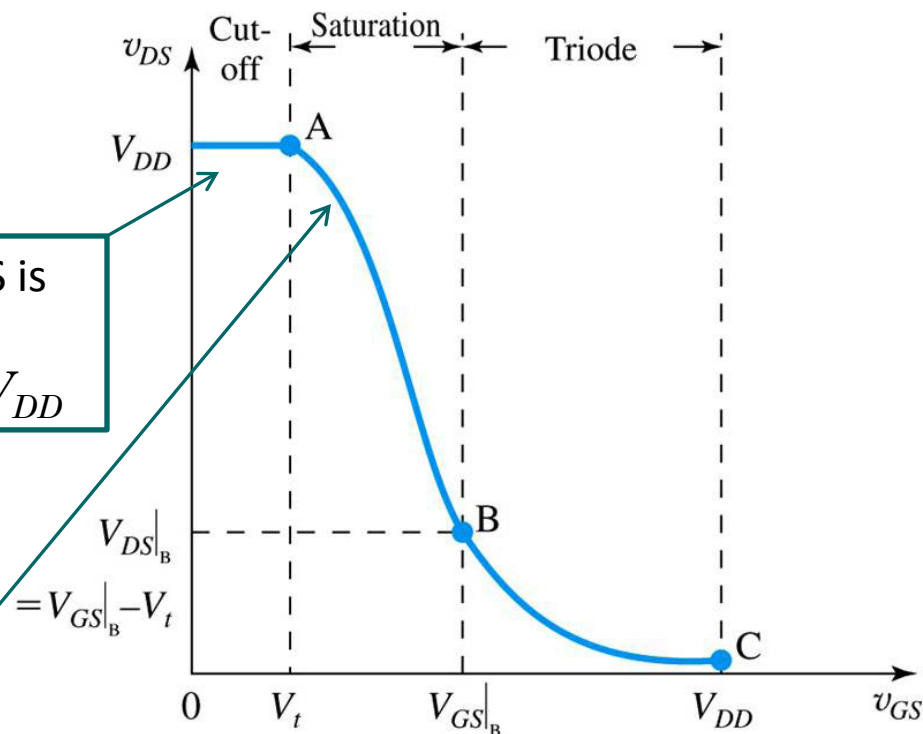
1) For $v_{GS} < V_t$, NMOS is in cutoff: $i_D = 0$ & $v_{DS} = V_{DD} - R_D i_D = V_{DD}$



2) Just to the right of point A:

- $V_{OV} = v_{GS} - V_t$ is small, so i_D is small.
- $v_{DS} = V_{DD} - R_D i_D$ is close to V_{DD}
- Thus, $v_{DS} > V_{OV}$ and NMOS is in saturation.

NMOS Transfer Function (2)

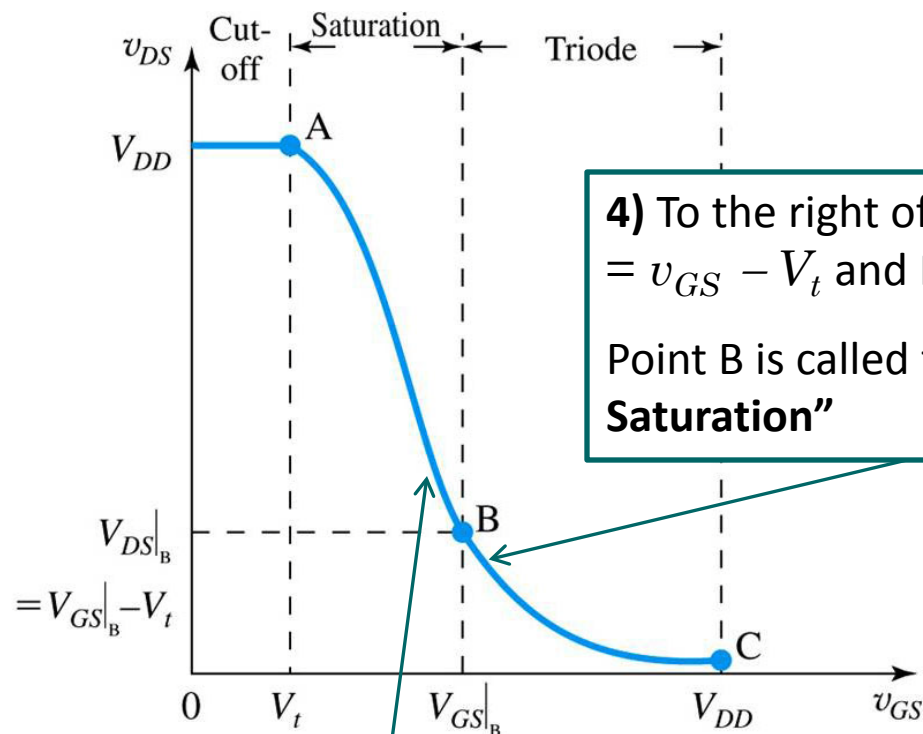

4) To the right of point B, $v_{DS} < V_{OV} = v_{GS} - V_t$ and NMOS enters triode. Point B is called the “**Edge of Saturation**”

3) As v_{GS} increases:


- $V_{OV} = v_{GS} - V_t$ and i_D become larger;
- $v_{DS} = V_{DD} - R_D i_D$ becomes smaller.
- At point B, $v_{DS} = V_{OV}$

NMOS Transfer Function (2)

1) For $v_{GS} < V_t$, NMOS is in cutoff: $i_D = 0$ & $v_{DS} = V_{DD} - R_D i_D = V_{DD}$

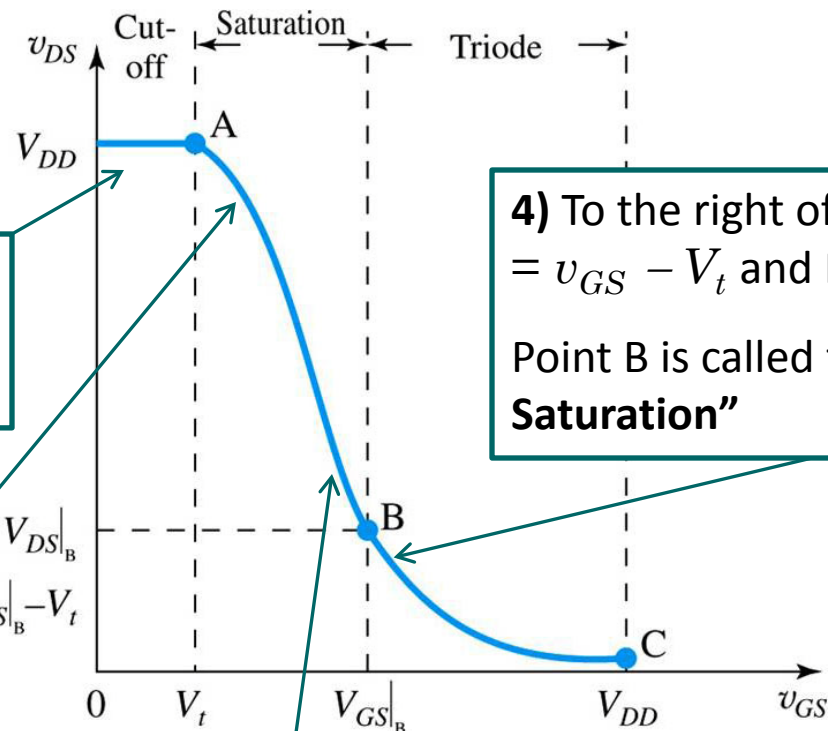2) Just to the right of point A:

- $V_{OV} = v_{GS} - V_t$ is small, so i_D is small.
- $v_{DS} = V_{DD} - R_D i_D$ is close to V_{DD}
- Thus, $v_{DS} > V_{OV}$ and NMOS is in saturation.




4) To the right of point B, $v_{DS} < V_{OV} = v_{GS} - V_t$ and NMOS enters triode. Point B is called the “Edge of Saturation”

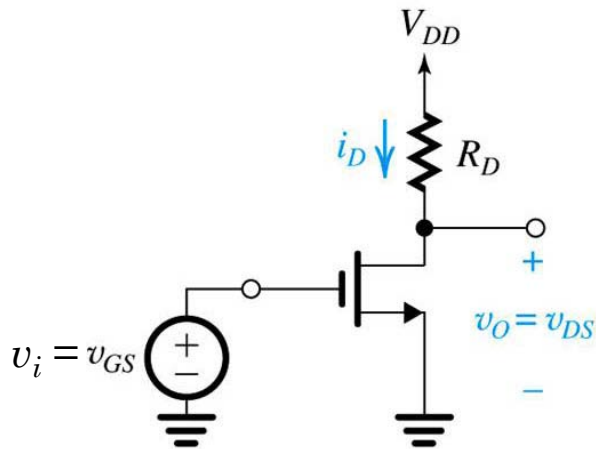3) As v_{GS} increases:


- $V_{OV} = v_{GS} - V_t$ and i_D become larger;
- $v_{DS} = V_{DD} - R_D i_D$ becomes smaller.
- At point B, $v_{DS} = V_{OV}$

Graphical analysis of NMOS Transfer Function (1)



NMOS i - v Characteristics: $i_D = f(v_{GS}, v_{DS})$


KVL: $V_{DD} = R_D i_D + v_{DS}$

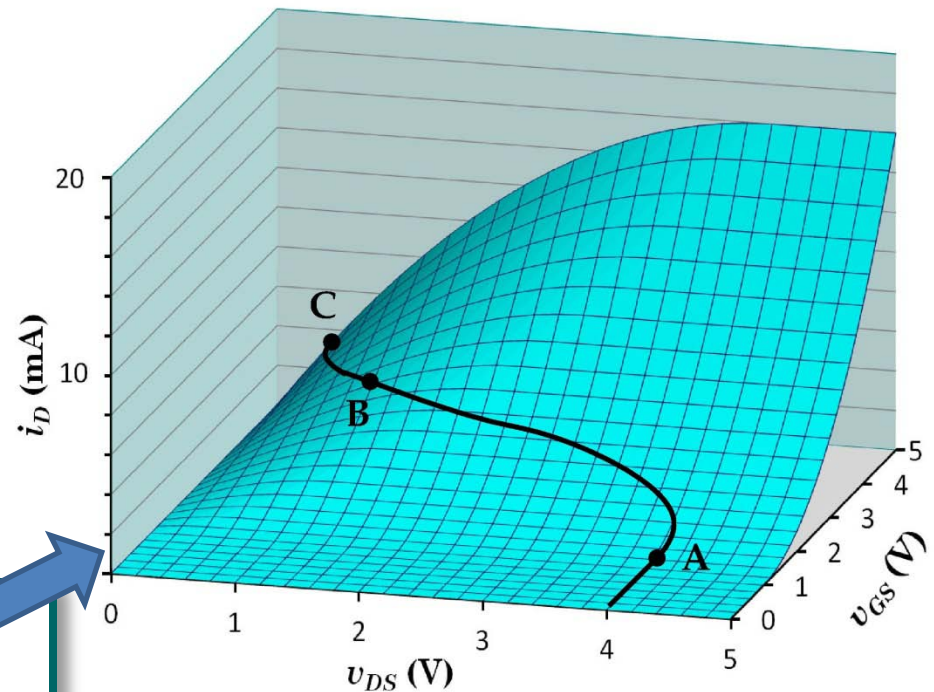


- KVL equation is a plane in this space.
- Intersection of KVL plane with the i v characteristics surface is a line.
- NMOS operating point is on this line (depending on the value of v_{GS} .)

- If we look from the bottom (i_D axis out of the paper), we can see the transfer function.

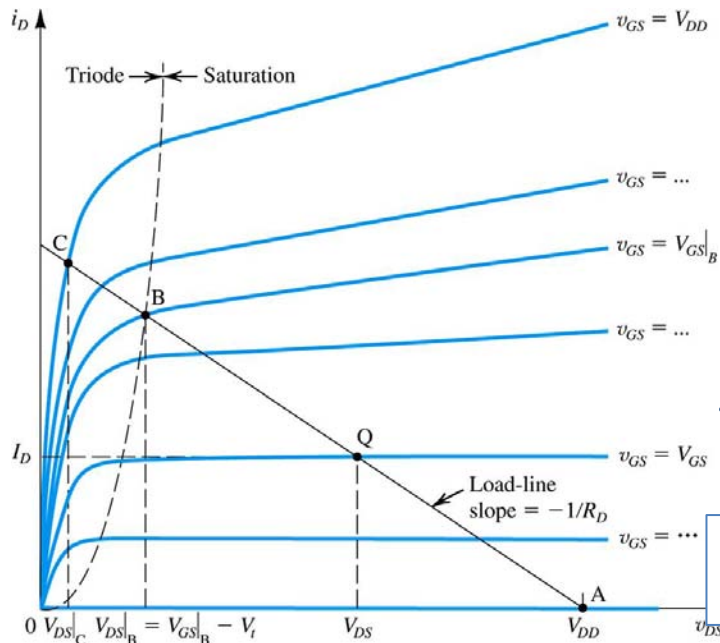
Graphical analysis of NMOS Transfer Function (6)



Looking parallel to v_{GS} axis

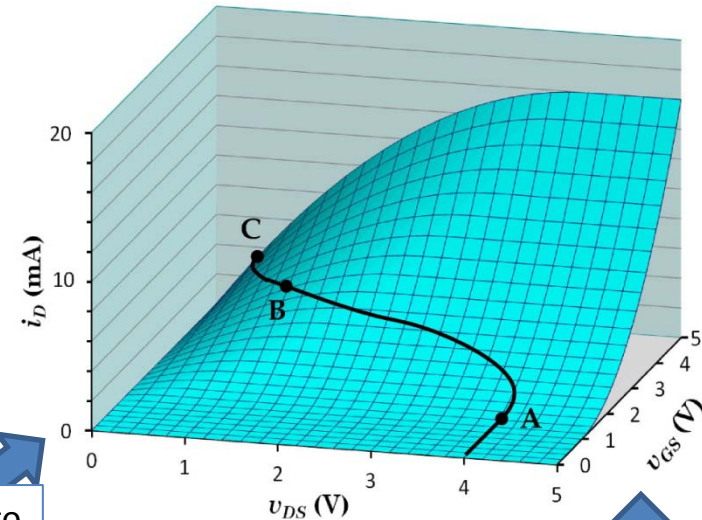


Looking from the bottom

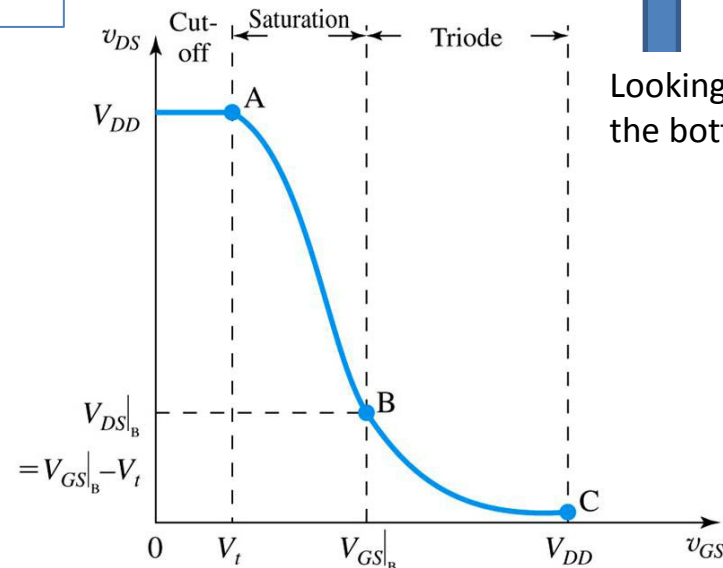

- Every point on the load line corresponds to a specific v_{GS} value.
- As v_{GS} increases, NMOS moves “up” the load line.


Foundation of Transistor Amplifiers (1)

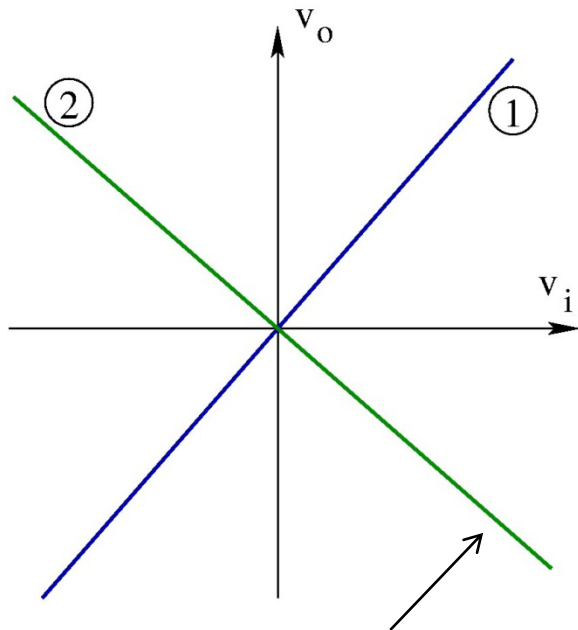- A voltage amplifier requires $v_o/v_i = \text{const.}$ (2 examples below)



- v_o/v_i can be negative (minus sign represents a 180° phase shift)


- MOS transfer function is NOT linear

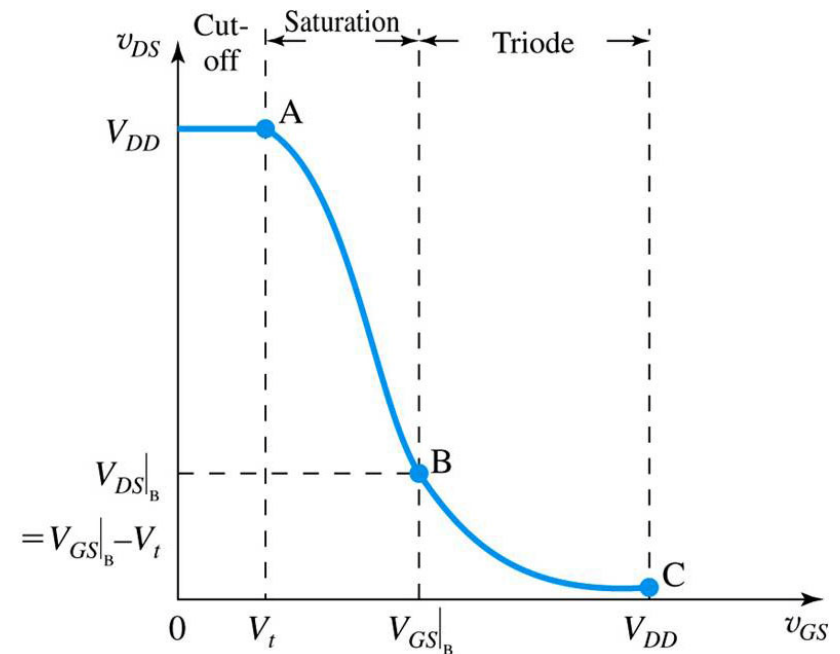

- In saturation, however, transfer function looks linear (but shifted)

Foundation of Transistor Amplifiers (2)

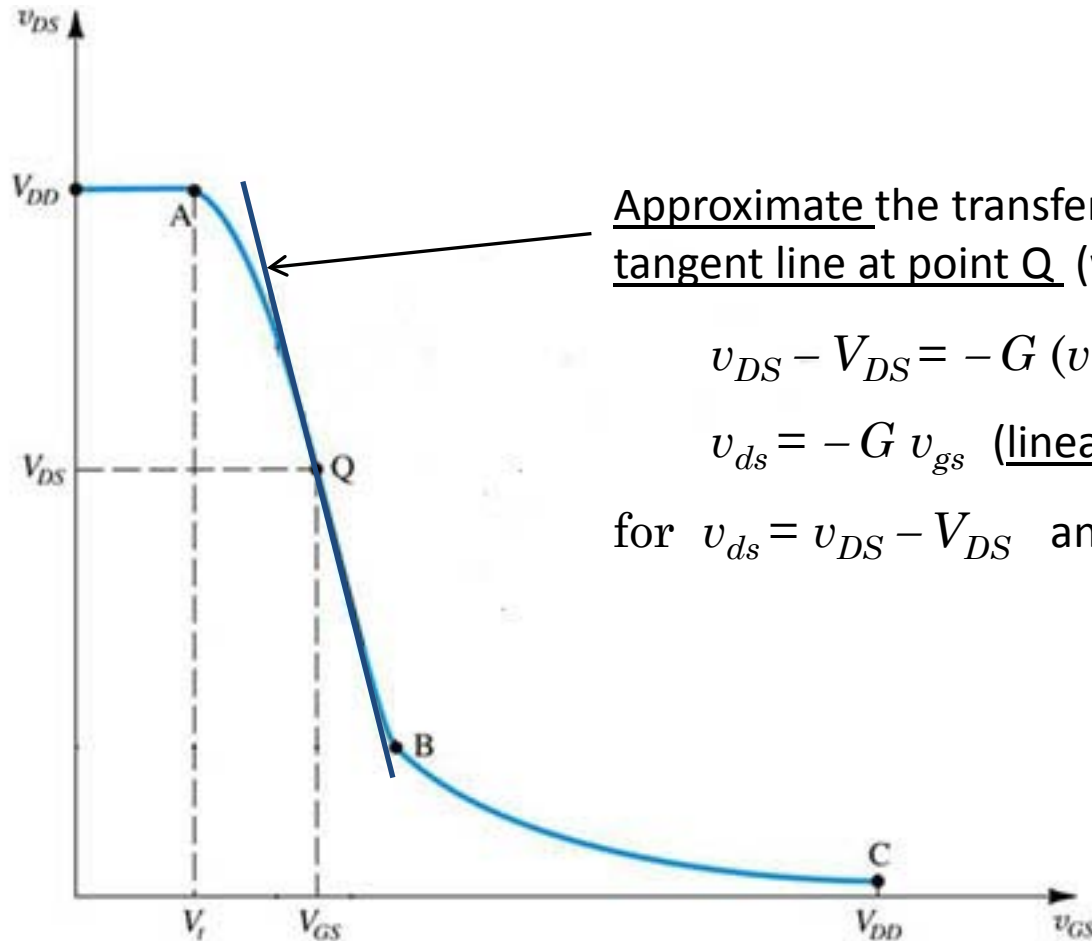➤ In saturation, transfer function appear to be linear



Approximate the transfer function with a tangent line at point Q (with a slope of $-G$):

$$v_{DS} - V_{DS} = -G (v_{GS} - V_{GS})$$

$$v_{ds} = -G v_{gs} \quad (\text{linear relationship})$$



for $v_{ds} = v_{DS} - V_{DS}$ and $v_{gs} = v_{GS} - V_{GS}$

Foundation of Transistor Amplifiers (3)



- Let us consider the response if NMOS remains in saturation at all times and v_{GS} is a combination of a constant value (V_{GS}) and a signal (v_{gs}).




$$v_{GS} = V_{GS} + v_{gs}$$

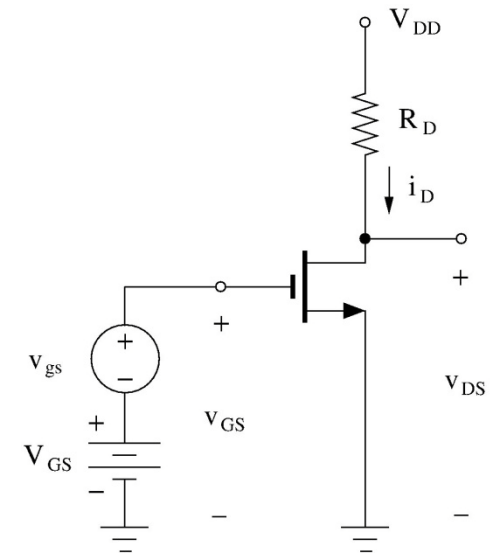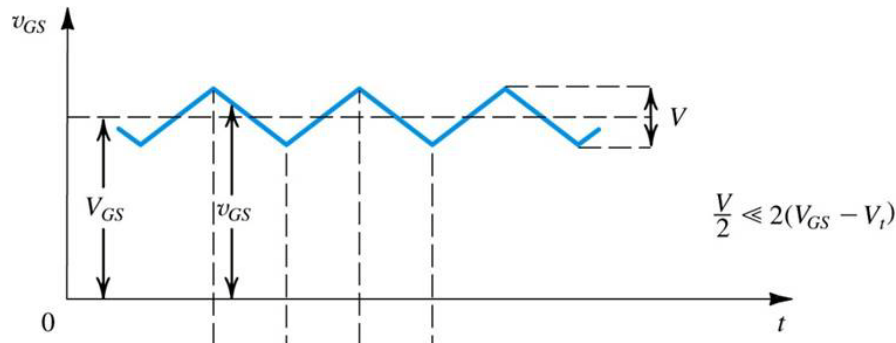

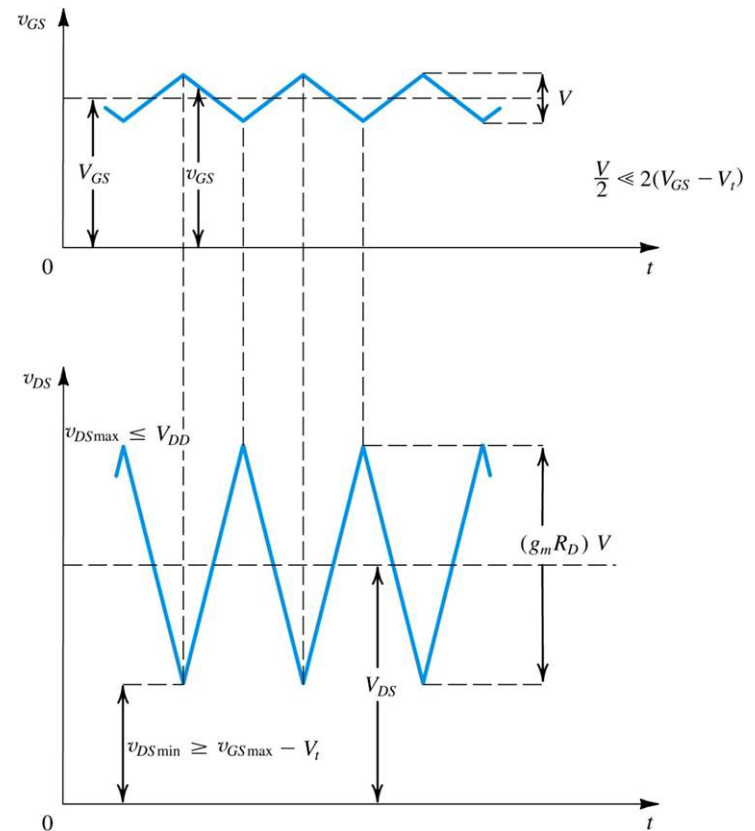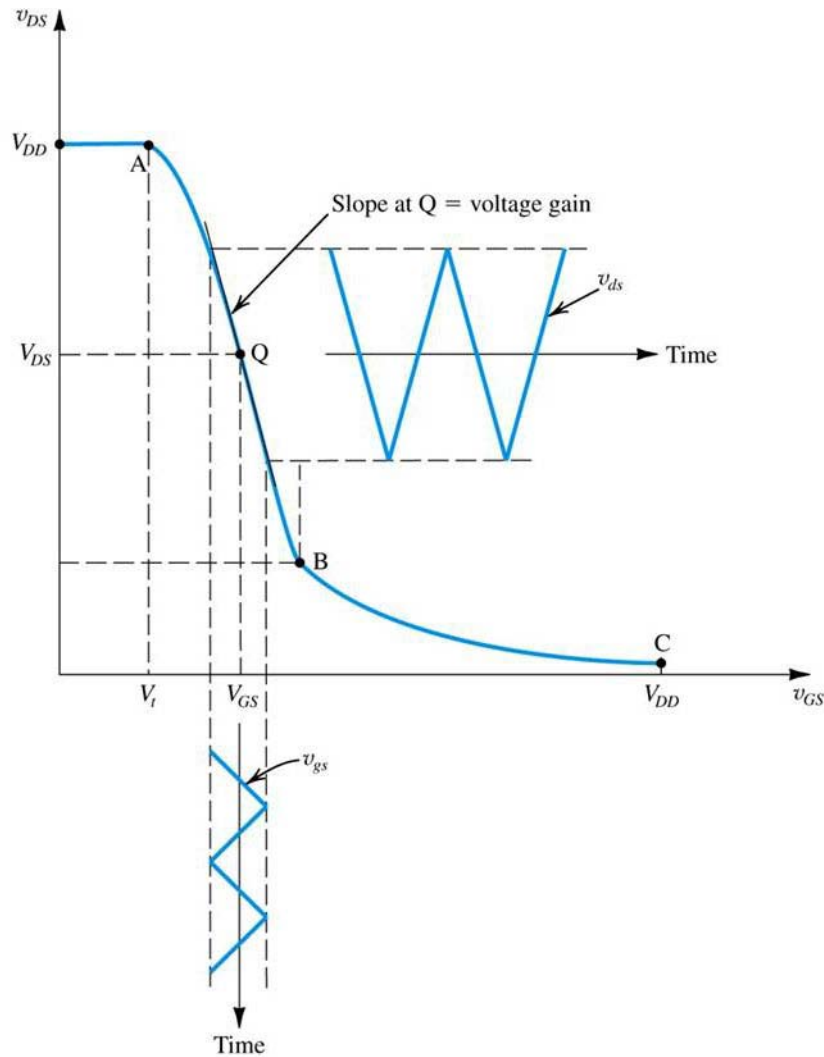The response to a combination of $v_{GS} = V_{GS} + v_{gs}$ can be found from the transfer function



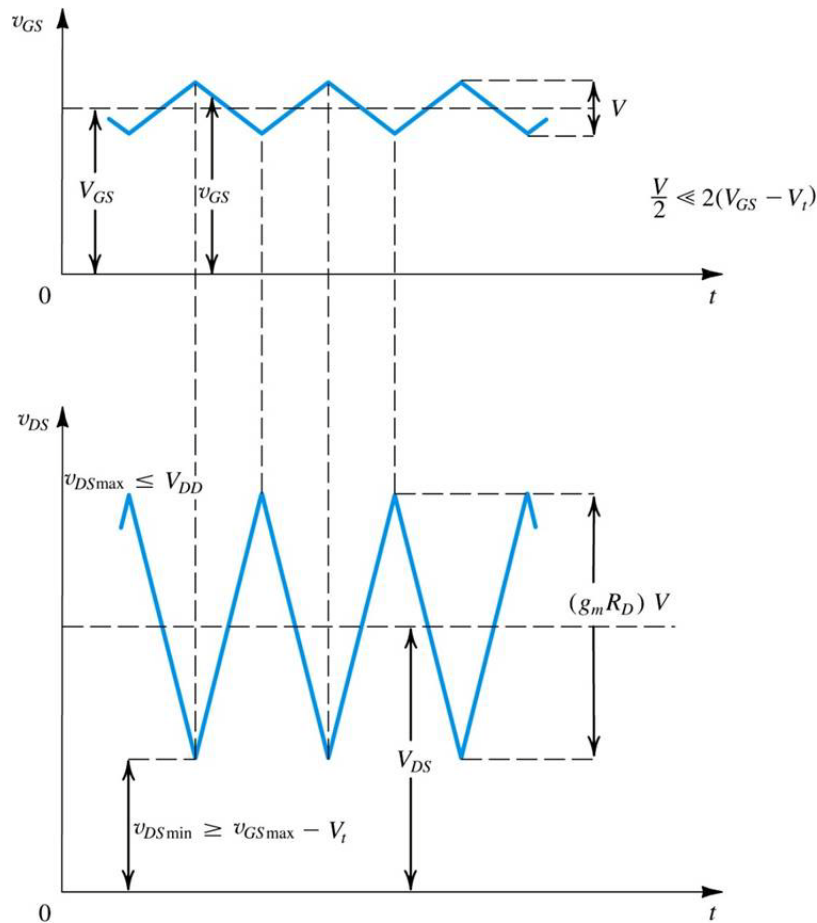Response to the signal appears to be linear



- Response ($v_o = v_{DS}$) is also made of a constant part (V_{DS}) and a signal response part (v_{ds}).
- Constant part of the response, V_{DS} , is ONLY related to V_{GS} , the constant part of the input (Q point on the transfer function of previous slide).
 - i.e., if $v_{gs} = 0$, then $v_{ds} = 0$
- The shape of the time varying portion of the response (v_{ds}) is similar to v_{gs} .
 - i.e., v_{ds} is proportional to the input signal, v_{gs}

Although the overall response is non-linear, the **transfer function for the signal is linear!**


Constant:
Bias

Signal and
response

$$\begin{aligned}v_{GS} &= V_{GS} + v_{gs} \\v_{DS} &= V_{DS} + v_{ds} \\i_D &= I_D + i_d\end{aligned}$$

Non-linear
relationship among
these parameters

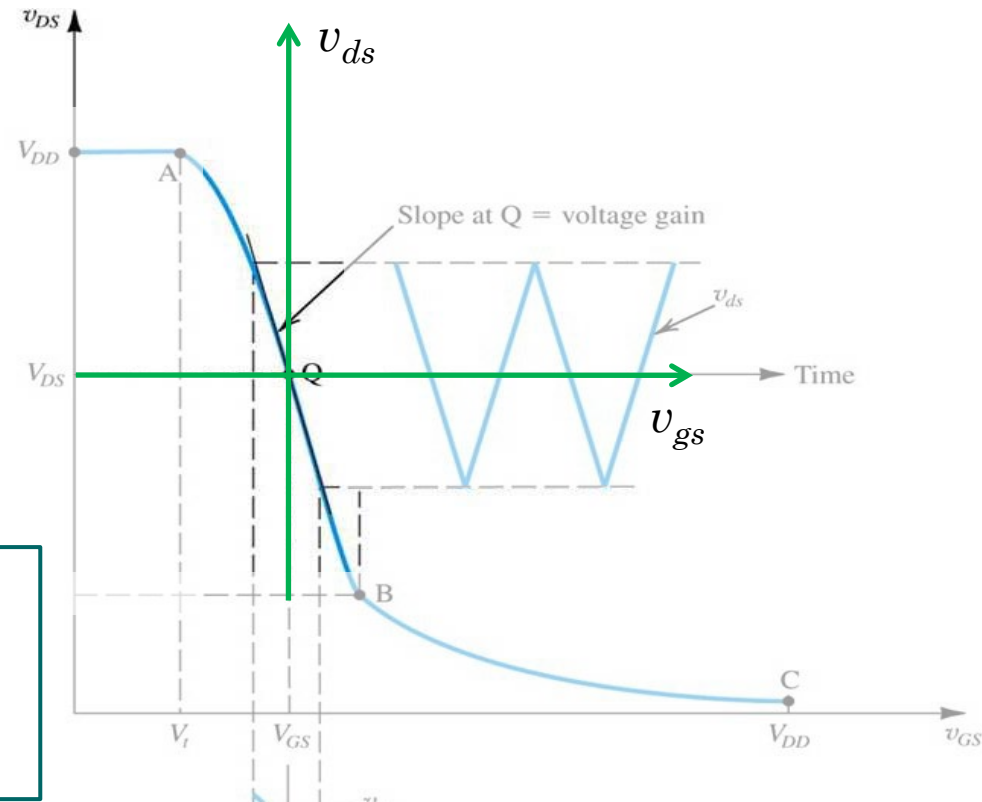Approximately
Linear
relationship among
these parameters



Important Points and Definitions!

- **Signal:** We want the response of the circuit to this input.
- **Bias:** State of the system when there is no signal.
 - Bias is constant in time (may vary extremely slowly compared to signal)
 - Purpose of the bias is to ensure that MOS is in saturation at all times.
- **Response** of the circuit (and its elements) to the signal is different than its response to the Bias (or to Bias + signal):
 - Signal i_v characteristics of elements are different, i.e. relationships among v_{gs} , v_{ds} , i_d is different from relationships among v_{GS} , v_{DS} , i_D .
 - Signal transfer function of the circuit is different from the transfer function for **total input (Bias + signal)**.

Issues in developing a MOS amplifier:


- 1. Find the i_v characteristics of the elements for the signal** (which can be different than their characteristics equation for bias).
 - This will lead to different circuit configurations for bias versus signal
- 2. Compute circuit response to the signal**
 - Focus on fundamental MOS amplifier configurations
- 3. How to establish a Bias point** (bias is the state of the system when there is no signal).
 - Stable and robust bias point should be resilient to variations in $\mu_n C_{ox} (W/L), V_t$, ... due to temperature and/or manufacturing variability.
 - Bias point details impact small signal response (e.g., gain of the amplifier).

Signal Circuit

- 1) We will find signal iv characteristics of various elements.
- 2) In order to use circuit theory tools, we will use the signal iv characteristics of various elements to assign a circuit symbol.
e.g.,
 - We will see that the diode signal iv characteristics is linear so for signals, diode can be modeled as a “circuit theory” resistor.
 - In this manner, we will arrive at a signal circuit.

Bias and Signal Circuits

Bias & Signal

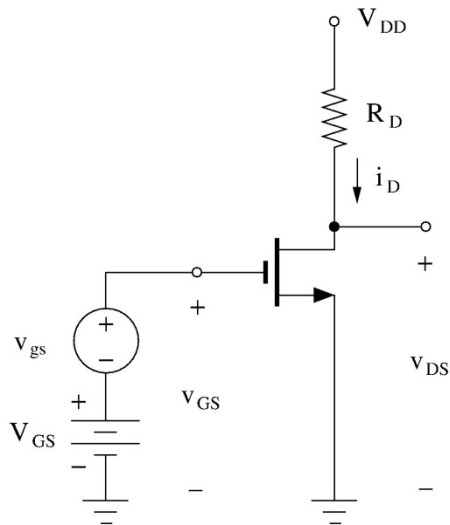


$$\text{MOS : } v_{GS}, v_{DS}, i_D, \\ (v_{GS} = V_{GS} + v_{gs}, \dots)$$

$$R_D : \quad v_R = V_R + v_r \\ i_R = I_R + i_r$$

.....

Bias

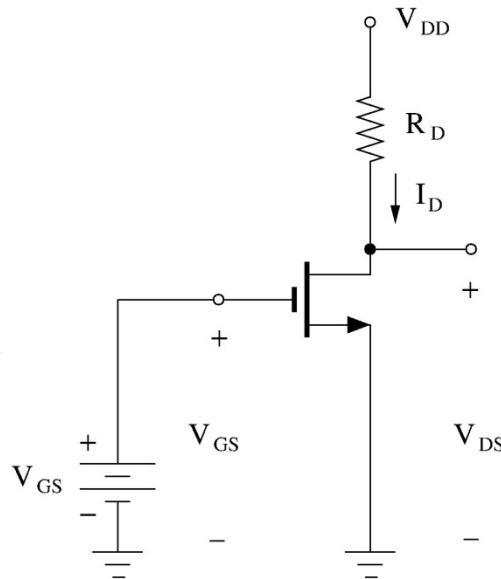


$$\text{MOS : } V_{GS}, V_{DS}, I_D,$$

$$R_D : \quad V_R, I_R$$

.....

Signal only
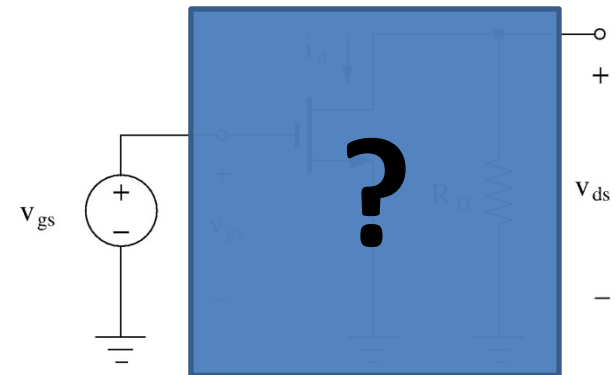
$$= (\text{Bias} + \text{Signal}) - \text{Bias}$$



$$\text{MOS : } v_{gs}, v_{ds}, i_d,$$

$$R_D : \quad v_r, i_r$$

.....

Finding signal circuit elements -- Resistor

Resistor	Voltage	Current	iv Equation
Bias + Signal:	v_R	i_R	$v_R = R i_R$
Bias:	V_R	I_R	$V_R = R I_R$
Signal:	$v_r = v_R - V_R$	$i_r = i_R - I_R$??



$$v_r = v_R - V_R = R i_R - R I_R = R (i_R - I_R) \quad \Rightarrow \quad v_r = R i_r$$

➤ A resistor remains as a resistor in the signal circuit.

Finding signal circuit elements – IVS & ICS

Independent voltage source	Voltage	Current	iv Equation
Bias + Signal:	v_{IVS}	i_{IVS}	$v_{IVS} = V_{DD} = const$
Bias:	V_{IVS}	I_{IVS}	$V_{IVS} = V_{DD} = const$
Signal:	$v_{ivs} = v_{IVS} - V_{IVS}$	$i_{ivs} = i_{IVS} - I_{IVS}$??

$$v_{ivs} = v_{IVS} - V_{IVS} = V_{DD} - V_{DD} = 0$$



$$v_{ivs} = 0, \quad i_{ivs} \neq 0$$



➤ **An independent voltage source becomes a short circuit!**

Similarly:

➤ **An independent current source becomes an open circuit!**

Exercise: Show that dependent sources remain as dependent sources

Summary of signal circuit elements

- **Resistors& capacitors:** The Same
 - Capacitor act as open circuit in the bias circuit.
- **Independent voltage source (e.g., V_{DD}) :** Effectively grounded
- **Independent current source:** Effectively open circuit
 - Careful about current mirrors as they are NOT “ideal” current sources (early effect and/or channel width modulation was ignored!)
- **Dependent sources:** The Same
- **Non-linear Elements:** Different!
 - Diodes & transistors ?

Formal derivation of small signal model

- Signal + Bias for element A (i_A, v_A) : $i_A = f(v_A)$
- Bias for element A (I_A, V_A) : $I_A = f(V_A)$
- Signal for element A (i_a, v_a) : $i_a = g(v_a)$

$$i_A = f(v_A)$$

$$= f(V_A) + f^{(1)}(V_A) \cdot (v_A - V_A) + \frac{f^{(2)}(V_A)}{2!} \cdot (v_A - V_A)^2 + \dots \quad (\text{Taylor Series Expansion})$$

$$= f(V_A) + f^{(1)}(V_A) \cdot v_a + \frac{f^{(2)}(V_A)}{2!} \cdot v_a^2 + \dots$$

$$\approx f(V_A) + f^{(1)}(V_A) \cdot v_a$$

$$i_A = i_a + I_A = I_A + f^{(1)}(V_A) \cdot v_a$$

$$i_a = g(v_a) = f^{(1)}(V_A) \cdot v_a$$

Small signal means:

$$\left| f^{(1)}(V_A) \cdot v_a \right| \gg \left| \frac{f^{(2)}(V_A)}{2!} \cdot v_a^2 \right|$$


$$\left| v_a \right| \ll 2 \cdot \left| \frac{f^{(1)}(V_A)}{f^{(2)}(V_A)} \right|$$

Small signal model vs i_v characteristics

Small signal model is equivalent to approximating the non-linear i_v characteristics curve by a line tangent to the i_v curve at the bias point

$$i_d = f^{(1)}(V_D) \times v_d$$
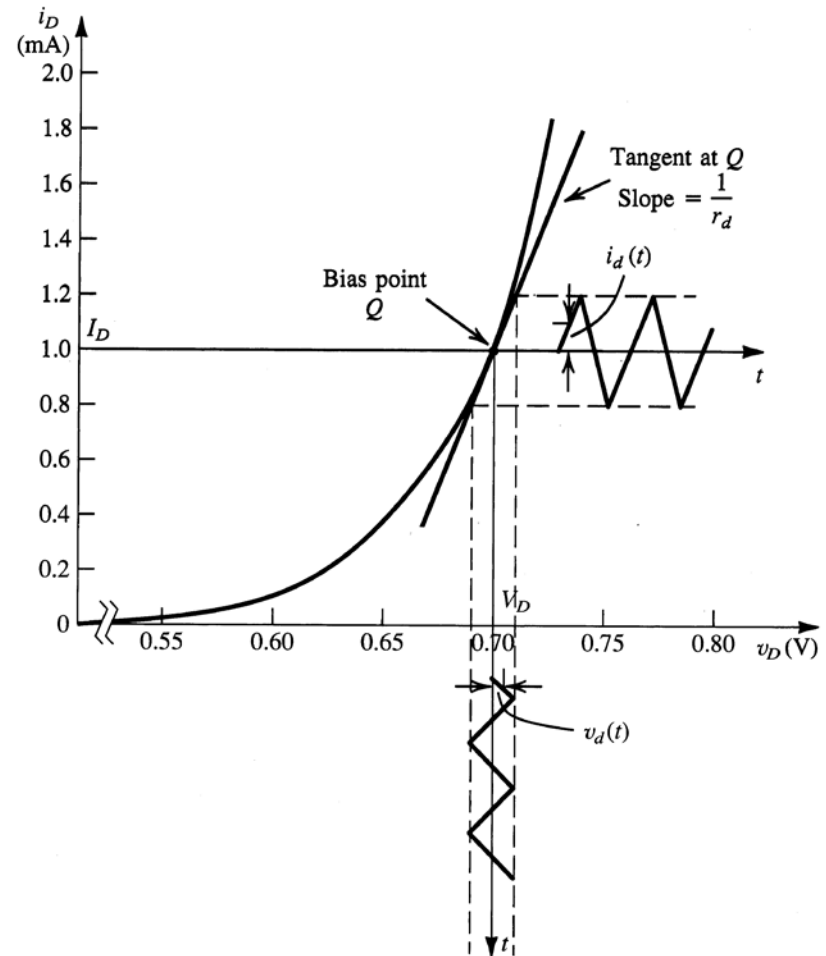
$$r_d = \frac{1}{f^{(1)}(V_D)} \approx \frac{nV_T}{I_D}$$



Derivation of MOS small signal model (1)

$$\text{MOS iv equations: } \begin{aligned} i_D &= f(v_{GS}, v_{DS}) \\ i_G &= 0 \end{aligned}$$

- Signal + Bias for MOS (i_D, v_{GS}, v_{DS}) : $i_D = f(v_{GS}, v_{DS}), \quad i_G = 0$
- Bias for MOS (I_D, V_{GS}, V_{DS}) : $I_D = f(V_{GS}, V_{DS}), \quad I_G = 0$
- Signal for MOS (i_d, v_{gs}, v_{ds}) : $i_d = g(v_{gs}, v_{ds}), \quad i_g = 0$

$$I_D + i_d = i_D = f(v_{GS}, v_{DS}) \quad (\text{Taylor Series Expansion in 2 variables})$$

$$\begin{aligned} &= f(V_{GS}, V_{DS}) + \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \cdot (v_{GS} - V_{GS}) + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \cdot (v_{DS} - V_{DS}) + \dots \\ &\approx I_D + \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \times v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \times v_{ds} \end{aligned}$$



$$i_d \approx \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \times v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \times v_{ds}$$

Derivation of MOS small signal model (2)

$$i_D = 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) = f(v_{GS}, v_{DS})$$


$$i_d = \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} \cdot v_{gs} + \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} \cdot v_{ds}$$

$$\begin{aligned} \left. \frac{\partial f}{\partial v_{GS}} \right|_{V_{GS}, V_{DS}} &= 2 \times 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)(1 + \lambda v_{DS}) \Big|_{V_{GS}, V_{DS}} \\ &= 2 \times \frac{0.5\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})}{(V_{GS} - V_t)} = \frac{2I_D}{V_{OV}} \equiv g_m \end{aligned}$$


$$\begin{aligned} \left. \frac{\partial f}{\partial v_{DS}} \right|_{V_{GS}, V_{DS}} &= \lambda \times 0.5\mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \Big|_{V_{GS}, V_{DS}} \\ &= \lambda \times \frac{0.5\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})}{(1 + \lambda V_{DS})} = \frac{\lambda I_D}{(1 + \lambda V_{DS})} \approx \lambda I_D \equiv \frac{1}{r_o} \end{aligned}$$

$$i_d = g_m \cdot v_{gs} + \frac{v_{ds}}{r_o} \quad i_g = 0$$

MOS small signal “circuit” model

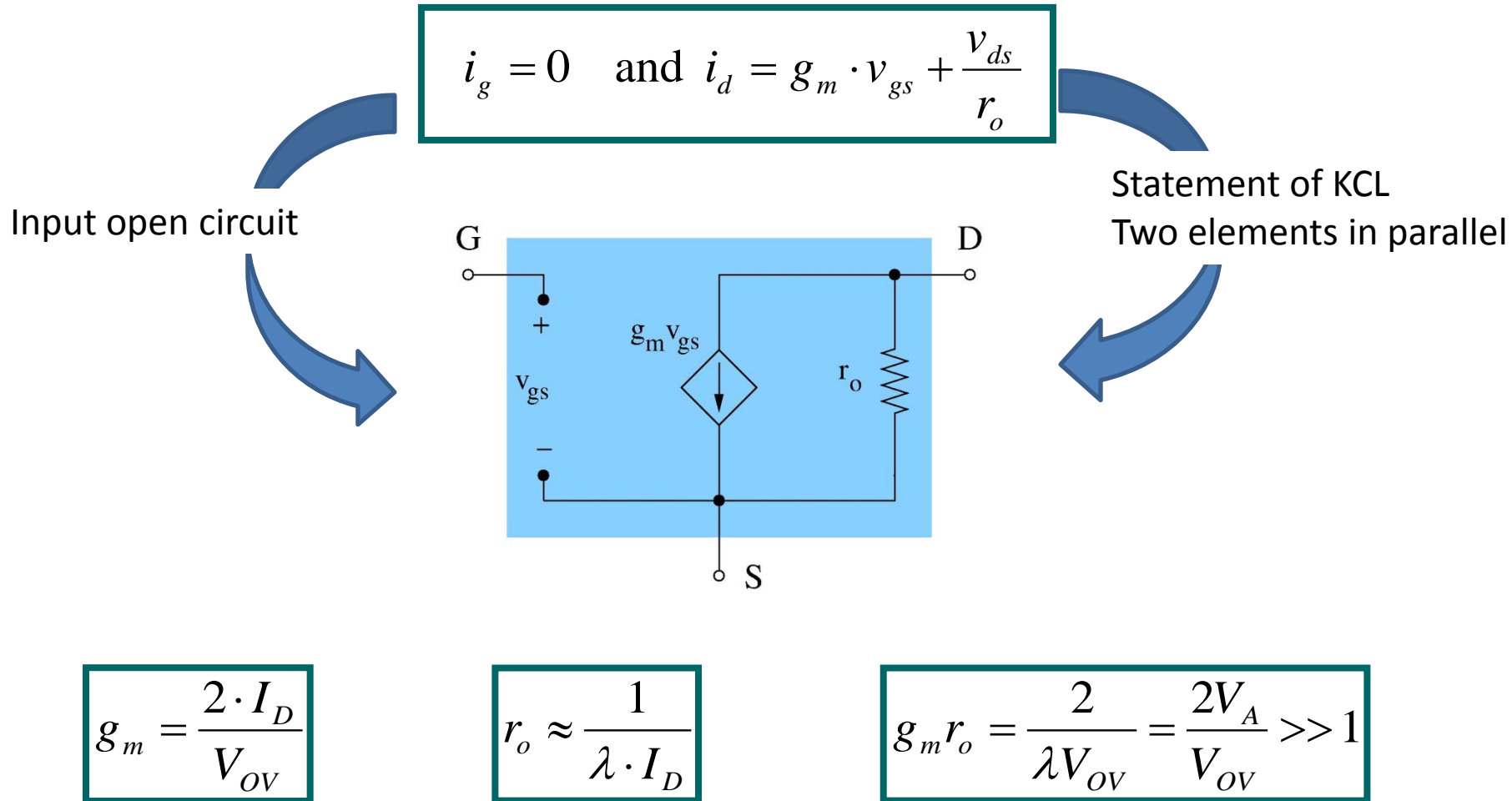

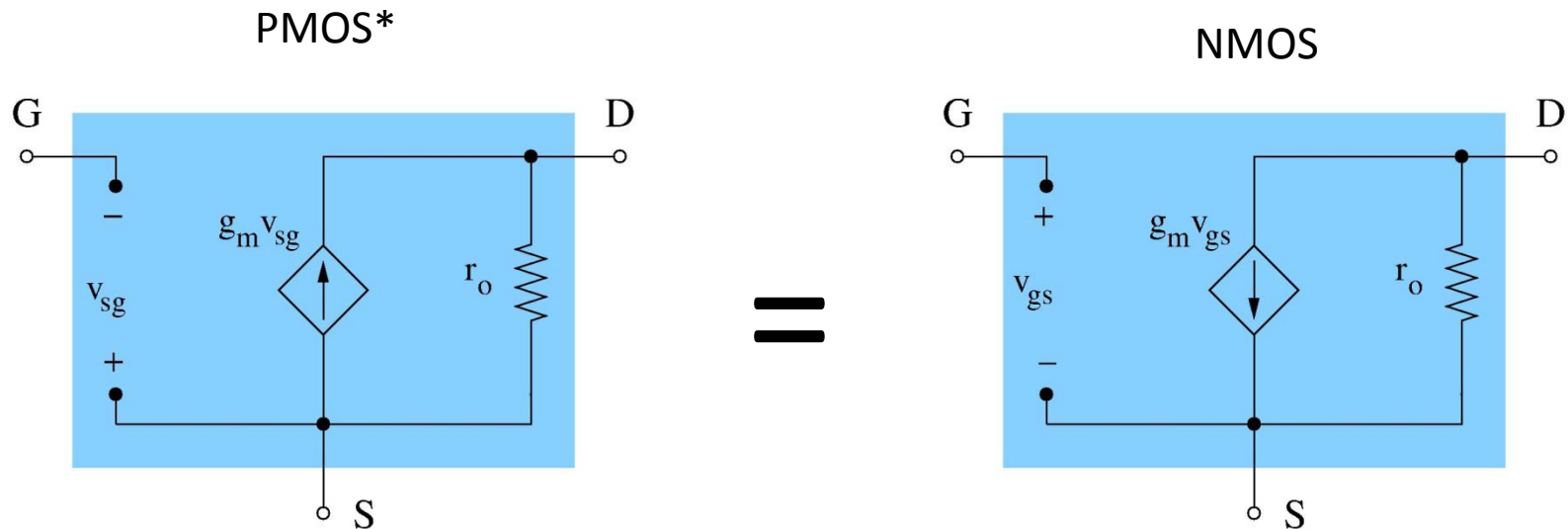PMOS small signal model is identical to NMOS



➤ PMOS small-signal circuit model is identical to NMOS

- We will use NMOS circuit model for both!
- For both NMOS and PMOS, while $i_D \geq 0$ and $I_D \geq 0$, signal quantities: i_d , v_{gs} , and v_{ds} , can be negative!