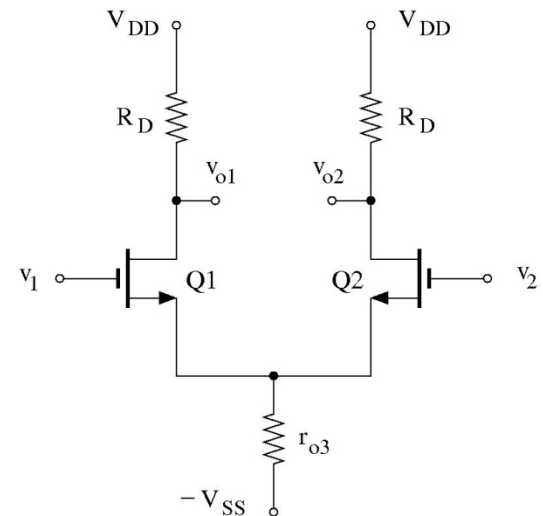




Differential Amplifiers: Implementation on ICs

Replacing R_{SS} and R_D with
current-sources and active loads



Resistor R_{ss} provides source degeneration for a stable bias


Bias (Common Mode circuit)

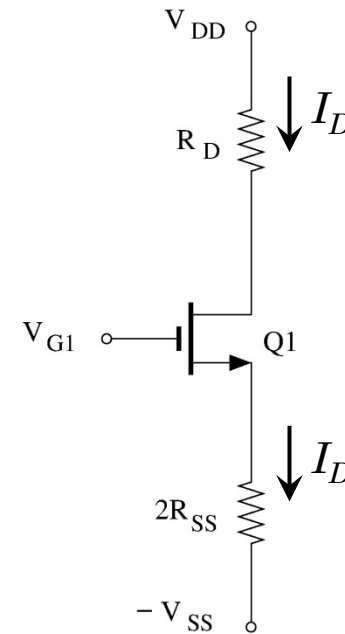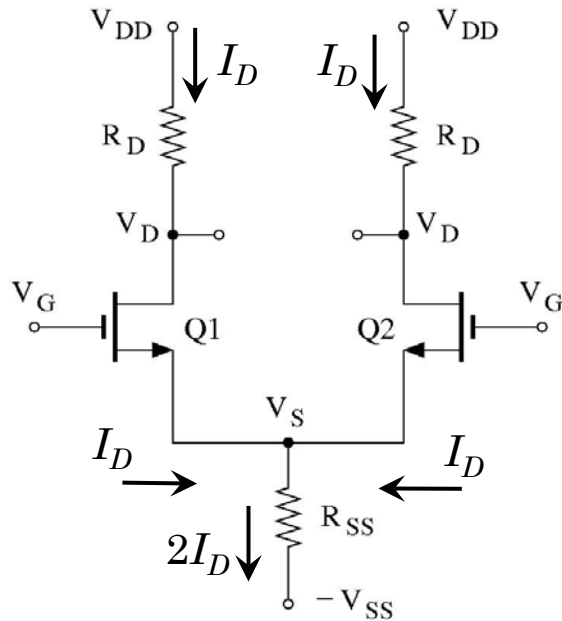

- In discrete circuits, bias is similar to that of a CS amplifier (source degeneration with a source resistor).
- **However** R_{SS} does not affect the differential gain and , in fact, should be large to improve CMRR (no need for a by-pass capacitor!)

Differential amplifier with current source active load

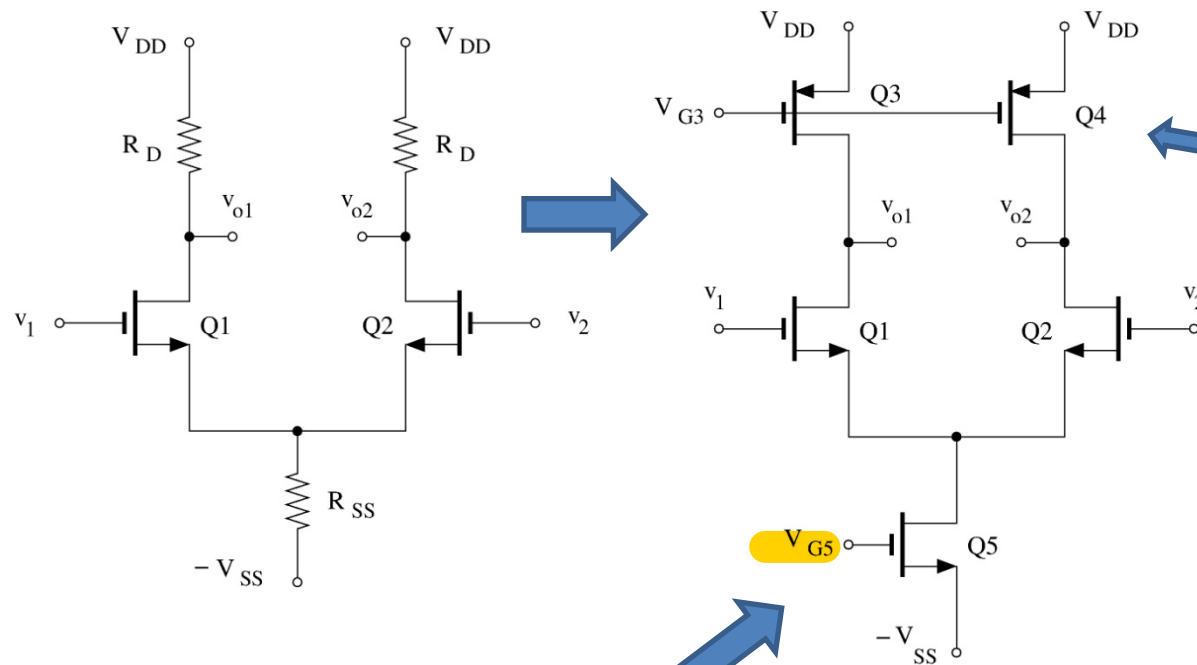Q1 and Q2 are identical & $V_{G2} = V_{G1}$




Q3 and Q4 are identical

- Q3/Q4 act **active load/ current source** (similar to a CS amplifier).

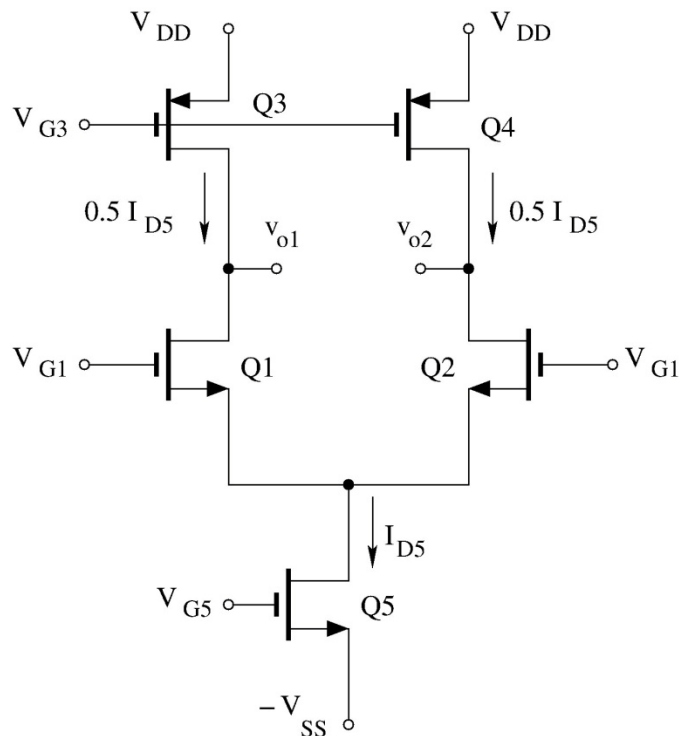Q5 is necessary

- For signals, Q5 provides $R_{SS} = r_{o5}$ necessary for **reducing common-mode gain** (a large $R_{SS} = r_{o5}$ can be obtained without significant voltage drop across Q5).
- Parameters of Q5 (i.e., W/L , V_G) **should be chosen such** that $I_{D3} = I_{D4} = 0.5 I_{D5}$.
- Q5 eases the **necessary precision in biasing Q1 and Q2 gates**.

Differential amplifier with current source active load – Bias



- Q1 and Q2 are identical & $V_{G2} = V_{G1}$
- Q3 and Q4 are identical
- Parameters of Q5 (i.e., W/L , V_G) are chosen such that $I_{D3} = I_{D4} = 0.5 I_{D5}$

$$V_{GS1} = V_{GS2} \Rightarrow V_{OV1} = V_{OV2}$$


$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = 0.5 I_{D5}$$

Ignoring channel-width modulation:*

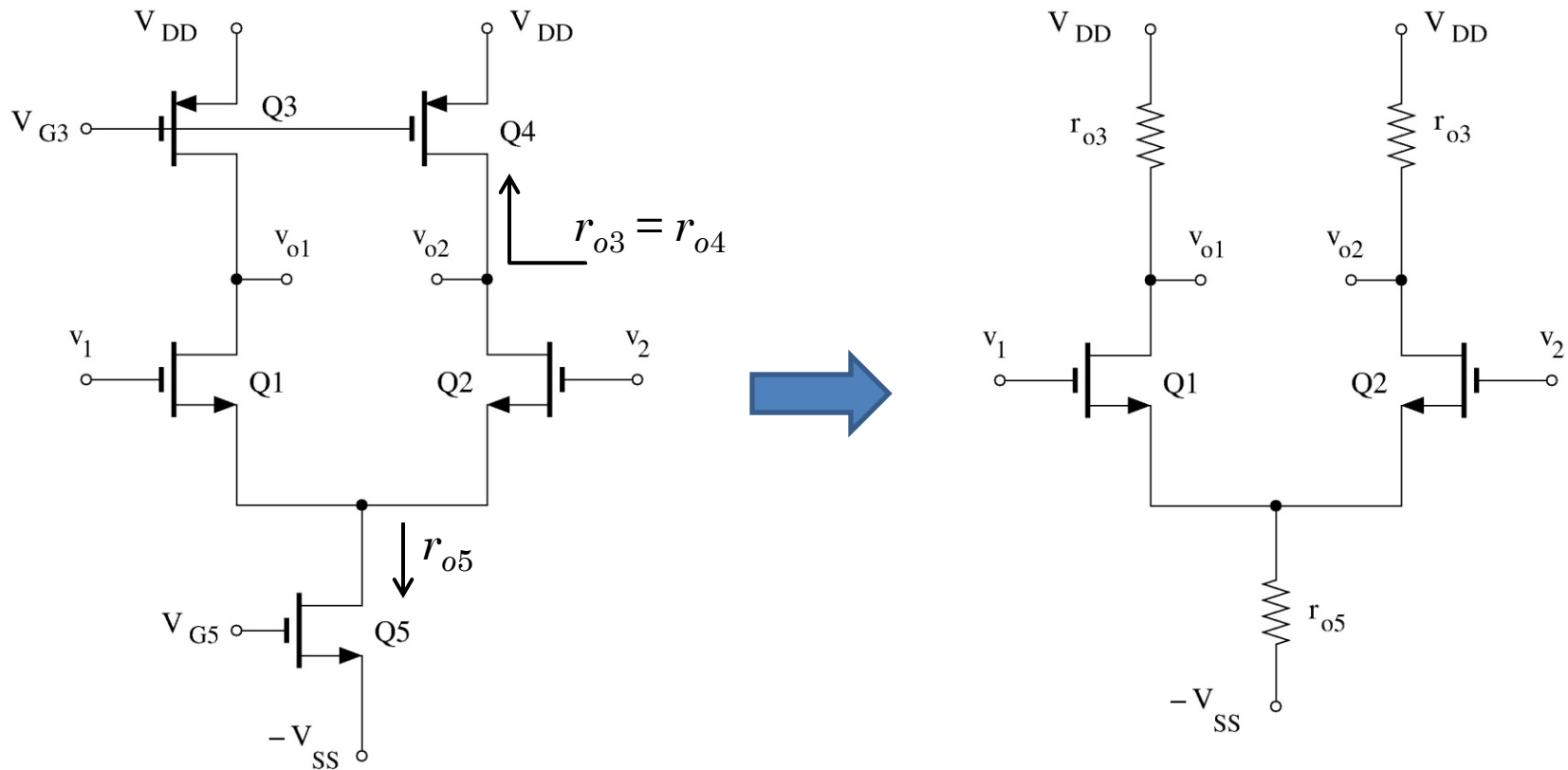
1. $I_{D1} = I_{D3} = 0.5 I_{D5}$ sets V_{OV1} and V_{GS1}
2. $V_{S1} = V_{GS1} - V_{G1}$
3. $V_{D5} = V_{S1}$
4. $V_{DS5} = V_{S1} + V_{SS}$
5. We need to include channel-width modulation to find V_{DS1} and V_{DS3}
6. Precise biasing of Q1 and Q2 are not necessary to get correct I_{D1} (it only affects V_{DS1} and V_{DS3})*

* Similar results are obtained if we do not ignore channel-width modulation: $V_S = V_{D5}$ will adjust to get the correct V_{GS1} and V_{OV1} (See problem set)

Differential amplifier with current source active load – Signal analysis



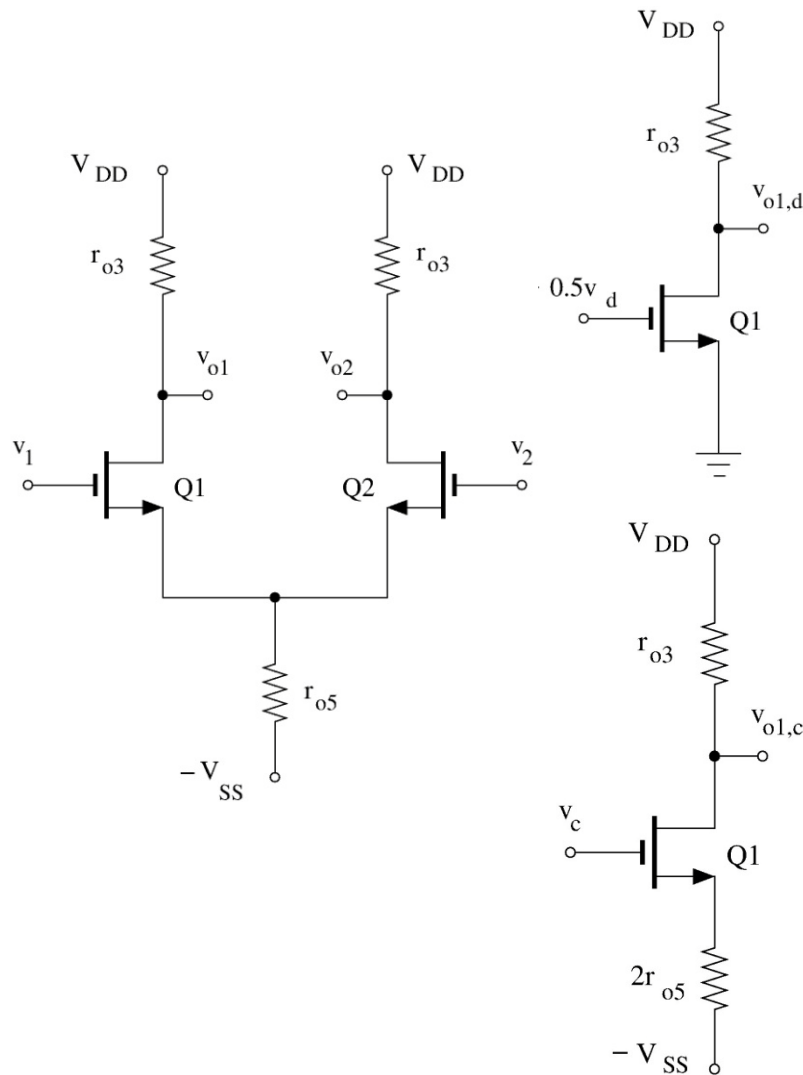Differential amplifier with current source active load – Signal analysis



Differential Mode

$$v_{o1,d} = -g_{m1}(r_{o1} \parallel r_{o3})(-0.5v_d) = 0.5g_{m1}(r_{o1} \parallel r_{o3})v_d$$


$$v_{o2,d} = -v_{o1} = -0.5g_{m1}(r_{o1} \parallel r_{o3})v_d$$

Common Mode

$$\frac{v_{o1,c}}{v_c} = -\frac{g_{m1}r_{o3}}{1 + 2g_{m1}r_{o5} + r_{o3}/r_{o1}}$$


$$v_{o1,c} = v_{o2,c}$$

Cascode differential amplifier

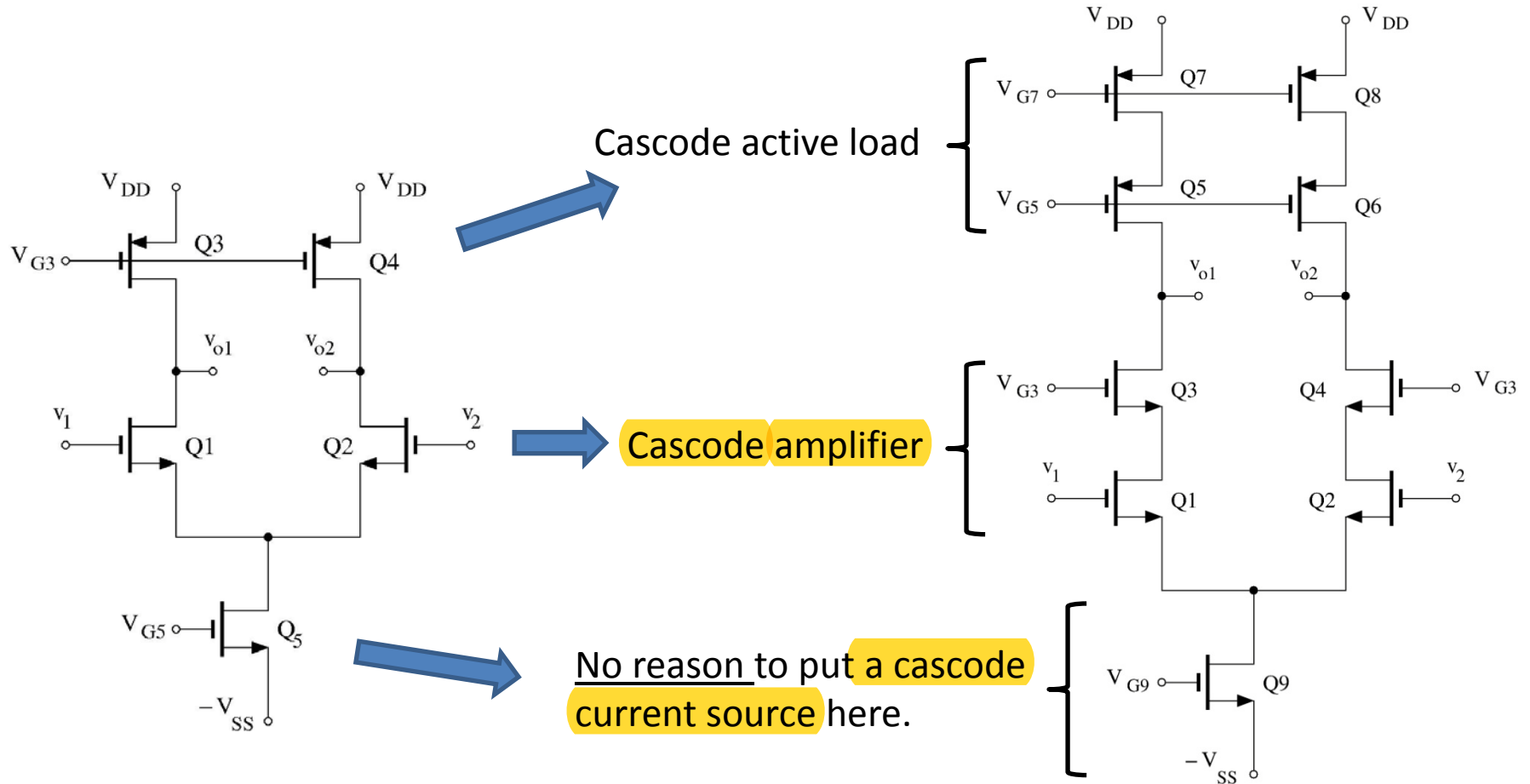


Bias analysis is similar to the case of differential amplifier with current-source active load.

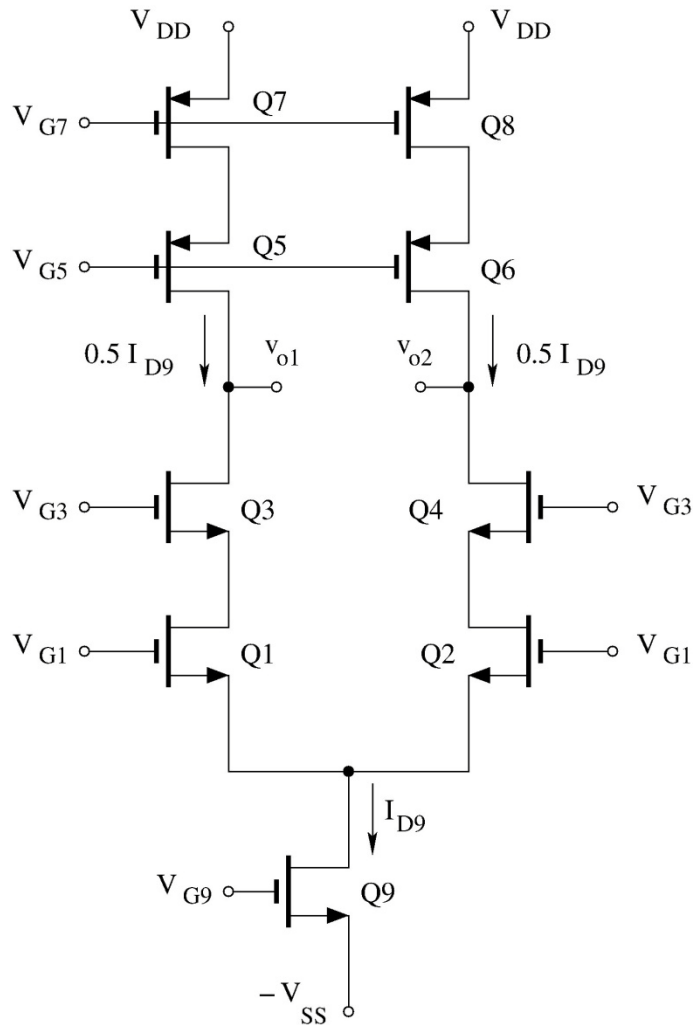Cascode differential amplifier – Signal analysis




Small
signal
→

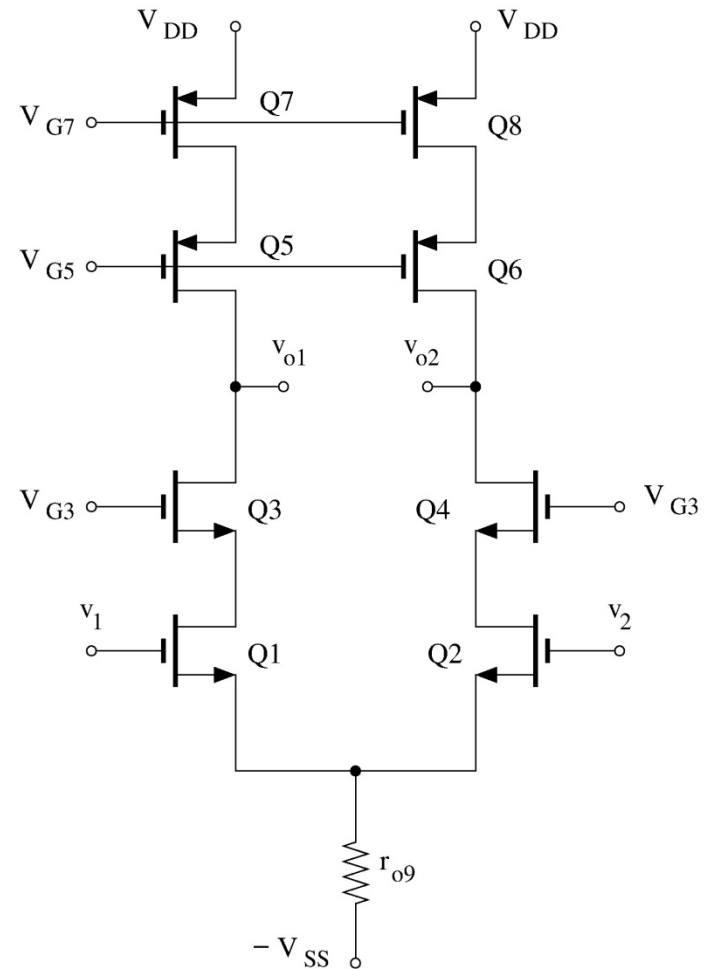

Cascode differential amplifier – Signal analysis

Differential Mode

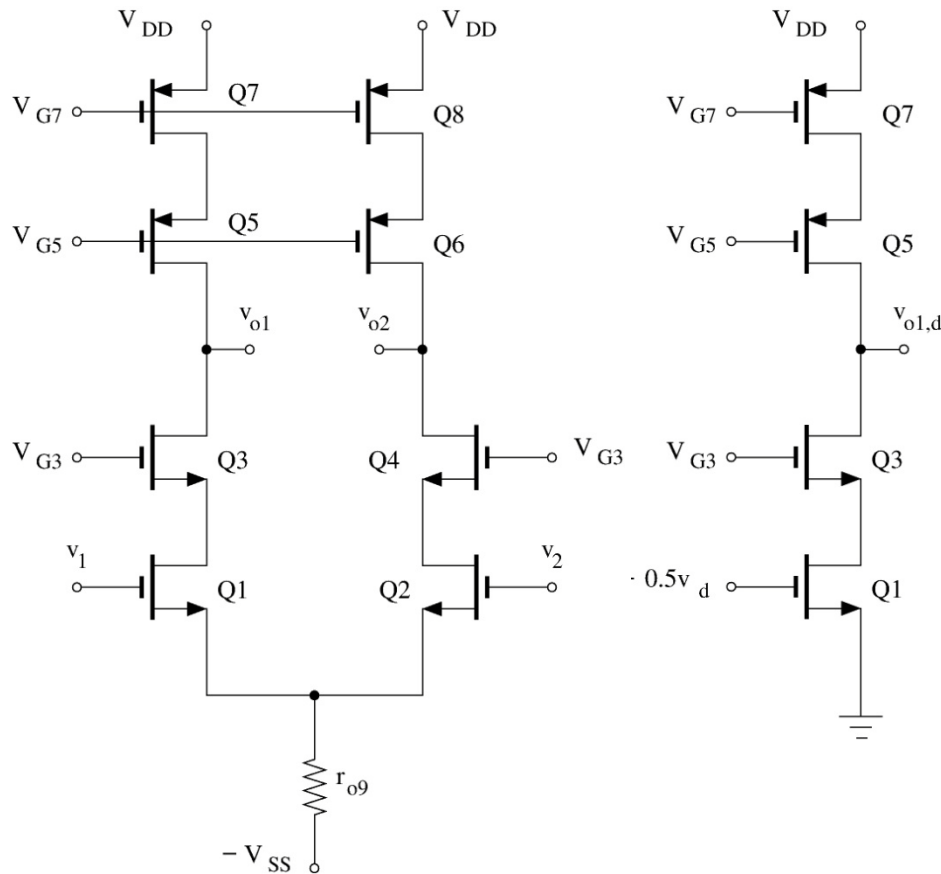

From Lecture Set 6:


$$v_{o1,d} \approx -\frac{g_{m1}g_{m3}g_{m5}r_{o1}r_{o3}r_{o5}r_{o7}}{g_{m3}r_{o1}r_{o3} + g_{m5}r_{o5}r_{o7}} \times (-0.5v_d)$$

$$= -g_{m1}(g_{m3}r_{o3}r_{o1} \parallel g_{m5}r_{o5}r_{o7})(-0.5v_d)$$

$$v_{o2,d} = -v_{o1,d}$$

Cascode differential amplifier – Signal analysis

Common Mode

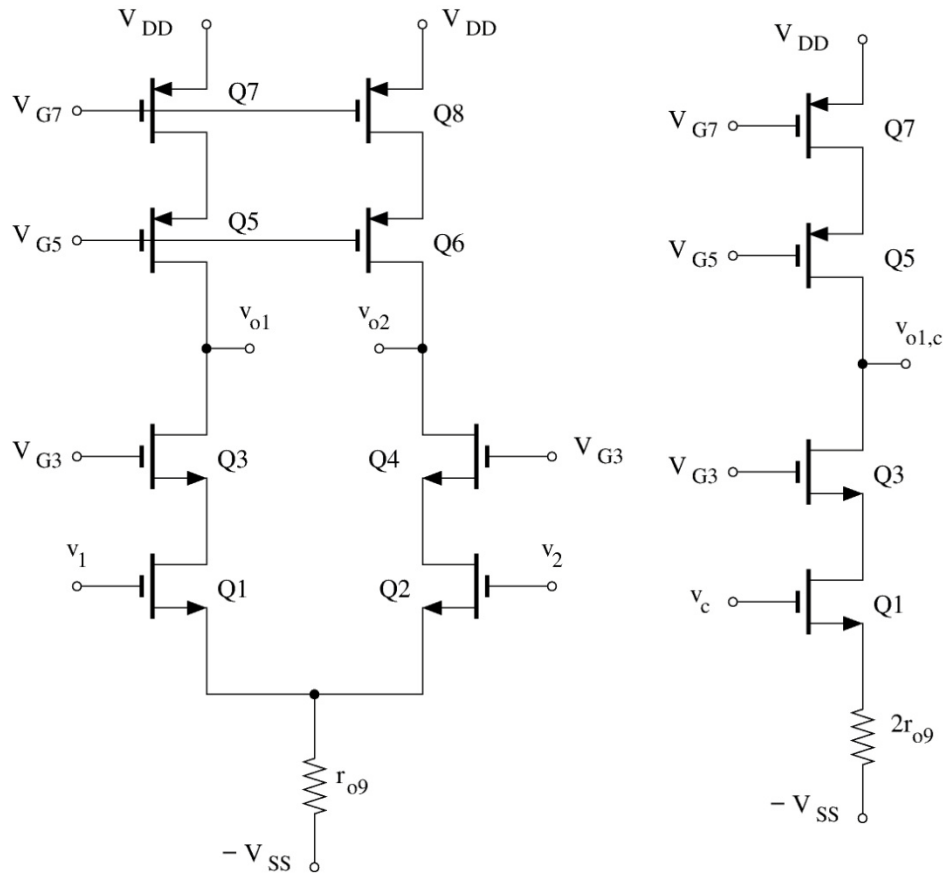


For $g_m r_o \gg 1^*$

$$v_{o2,c} = v_{o1,c} \approx -\frac{g_{m5} r_{o5} r_{o7}}{2r_{o9}} \times v_c$$

* Derive the expression for $v_{o1,c}$


Differential Amplifiers – Output Configurations

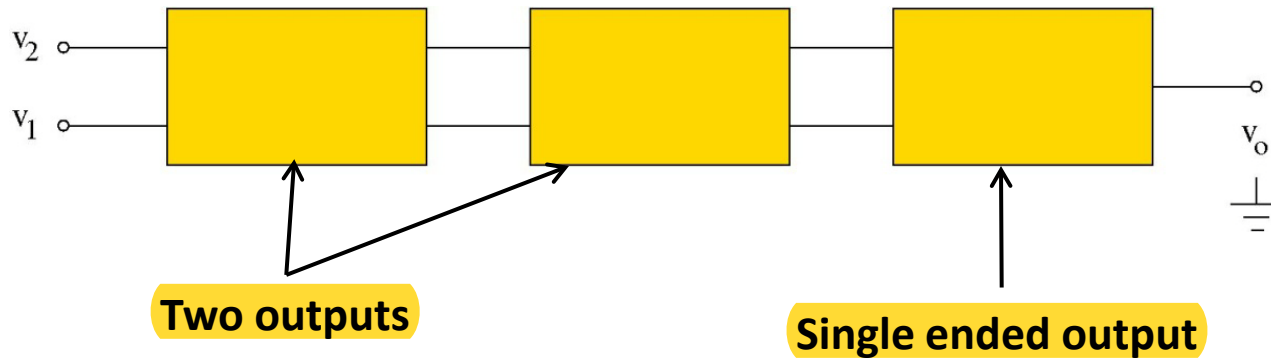Typical implementation of differential amplifier circuits




Output Configurations of Differential Amplifiers


Differential Output

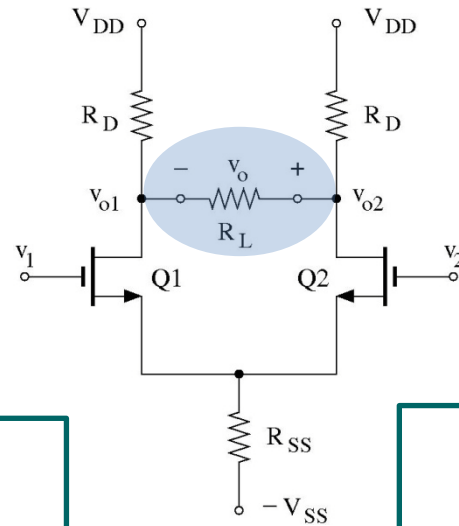

Single-ended Output


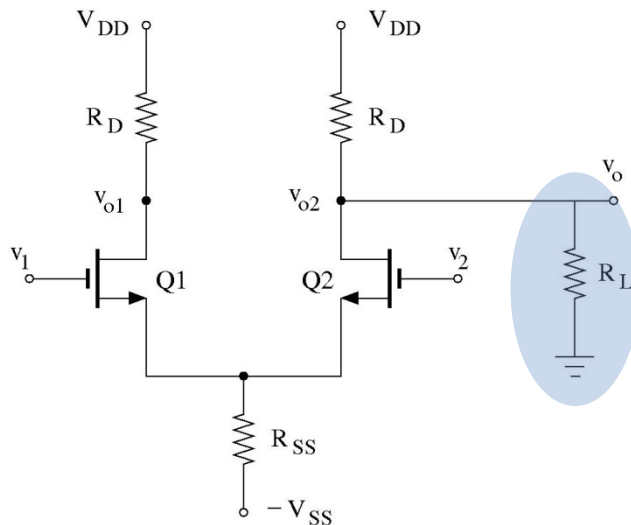


Two Separate Outputs

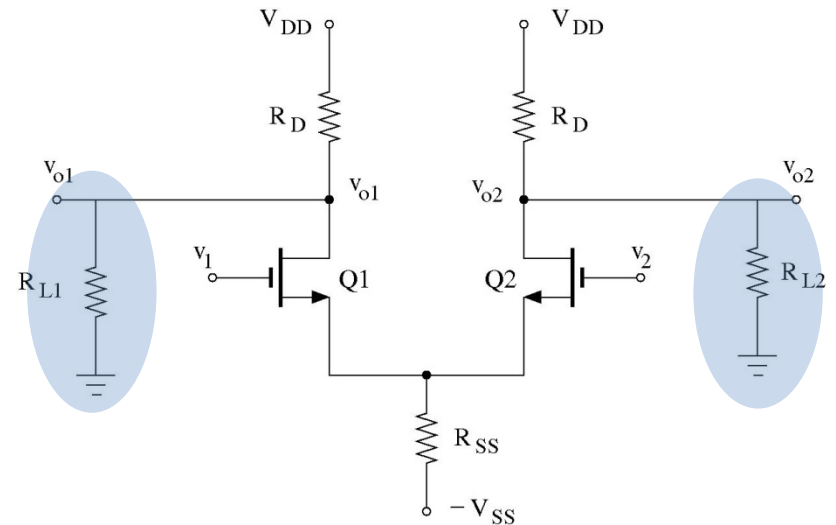


Differential Amplifiers with Differential Output


Differential Output

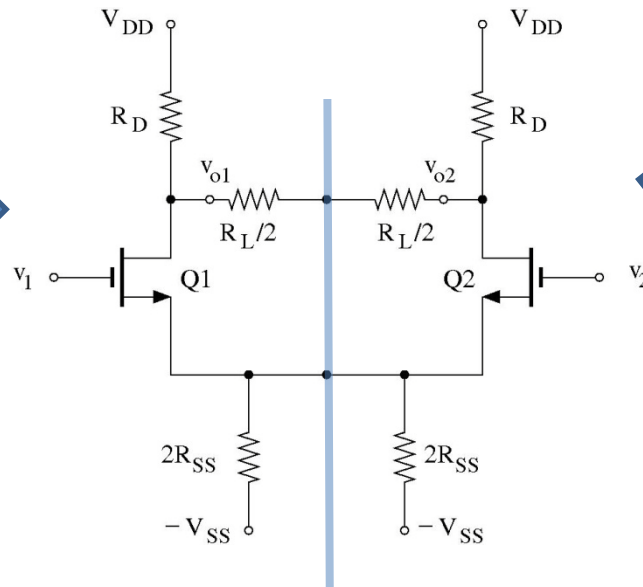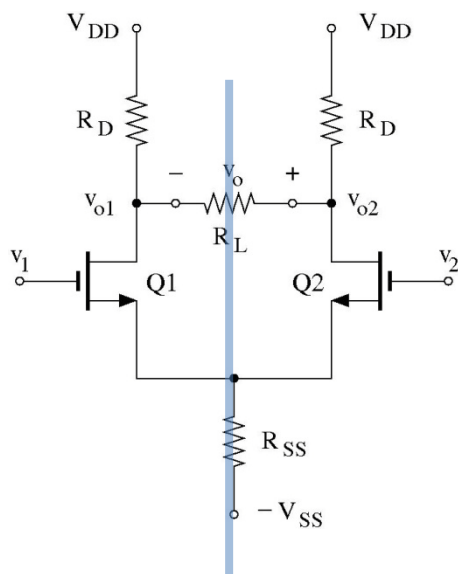

Differential Mode

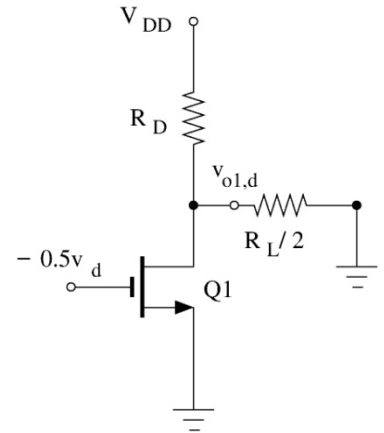


Common Mode

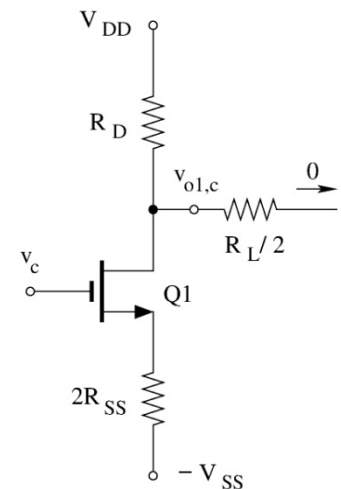

Not used often because the load floats
(i.e., not attached to the ground)


Differential Amplifiers with Differential Output

Differential Output

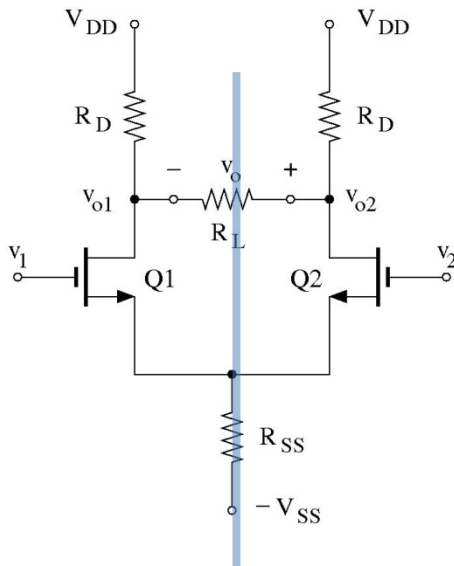

$$v_o = A_c \cdot v_c + A_d \cdot v_d$$

Differential Mode

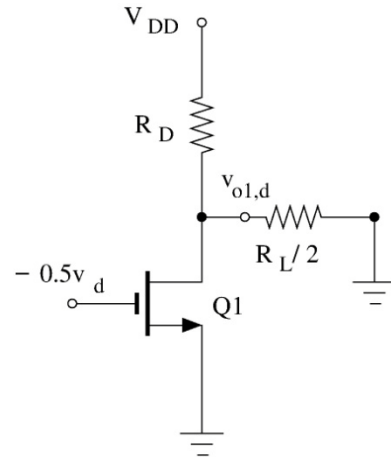


$$v_{o1,d} = -g_m (r_o \parallel R_D \parallel R_L/2) (-0.5v_d)$$

$$v_{o2,d} = -v_{o1,d}$$

$$v_{od} = v_{o2,d} - v_{o1,d} = -2v_{o1,d} = -g_m (r_o \parallel R_D \parallel R_L/2) v_d$$

$$A_d = \frac{v_{od}}{v_d} = -g_m (r_o \parallel R_D \parallel R_L/2)$$

Common Mode

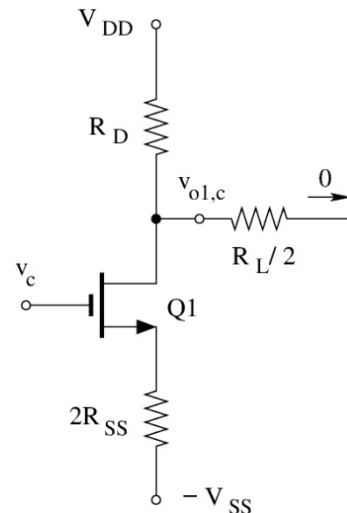

$$\frac{v_{o1,c}}{v_c} = -\frac{g_m R_D}{1 + 2g_m R_{SS} + R_D/r_o}$$

$$v_{o2,c} = v_{o1,c}$$


$$v_{oc} = v_{o2,c} - v_{o1,c} = 0$$

$$A_c = \frac{v_{oc}}{v_c} = 0$$

$$\text{CMRR} = \frac{|A_d|}{|A_c|} = \infty$$


Differential Amplifiers with Two Outputs

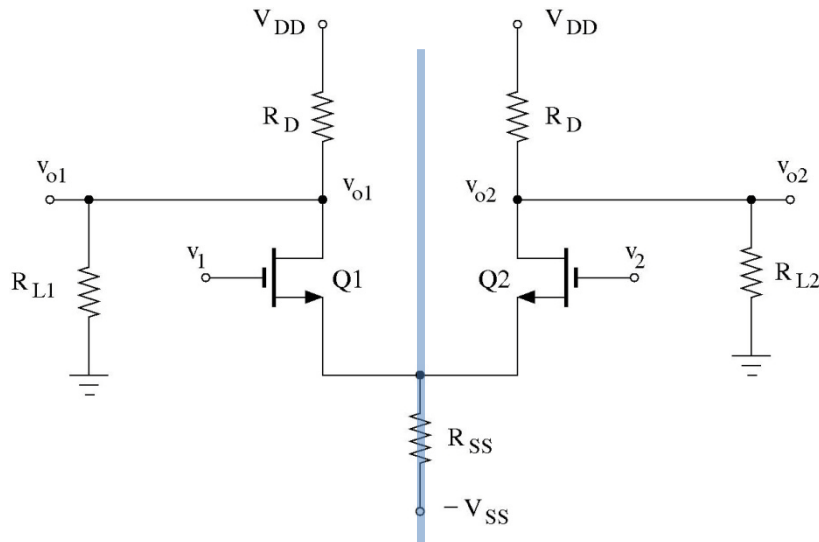Two Separate Outputs ($R_{L1} \approx R_{L2} = R_L$)
(i.e., input to another difference amplifier)




Note: To use half circuit, ($R_{L1} \approx R_{L2}$) or R_L should be large enough so that symmetry is preserved (i.e. $R_{L1,2} \gg R_o$)

Differential Mode

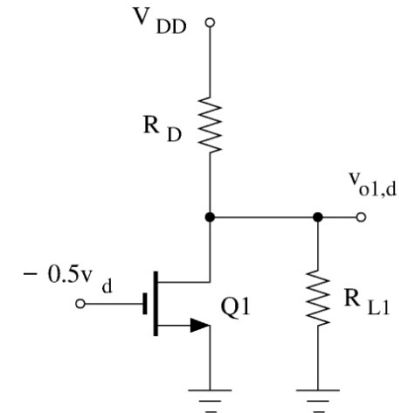


Common Mode

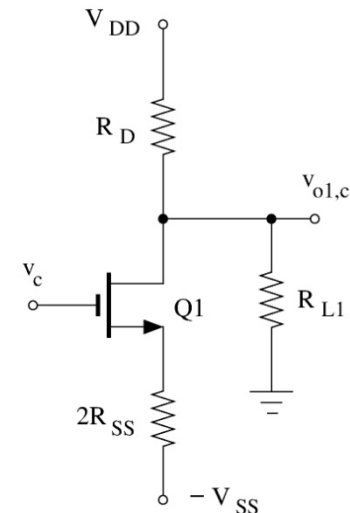

Differential Amplifiers with Two Outputs


Differential Mode

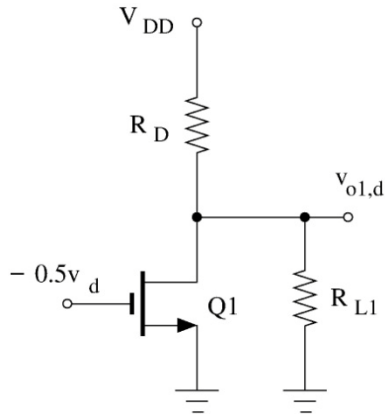

$$\frac{v_{o1,d}}{-0.5v_d} = -g_m(r_o \parallel R_D \parallel R_{L1})$$

$$\frac{v_{o2,d}}{+0.5v_d} = -g_m(r_o \parallel R_D \parallel R_{L2})$$

Common Mode

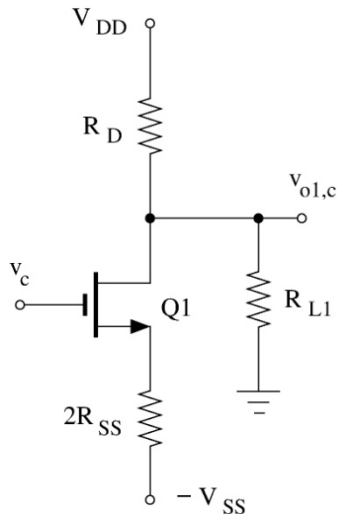

$$\frac{v_{o1,c}}{v_c} = -\frac{g_m(R_D \parallel R_{L1})}{1 + 2g_m R_{SS} + (R_D \parallel R_{L1})/r_o}$$


$$\frac{v_{o2,c}}{v_c} = -\frac{g_m(R_D \parallel R_{L2})}{1 + 2g_m R_{SS} + (R_D \parallel R_{L2})/r_o}$$

Note: Each output has its own differential- and common-mode gains:

$$A_{1d} = \frac{v_{o1,d}}{v_d}, \quad A_{1c} = \frac{v_{o1,c}}{v_c}$$



$$v_{o1} = A_{1c} \cdot v_c + A_{1d} \cdot v_d$$

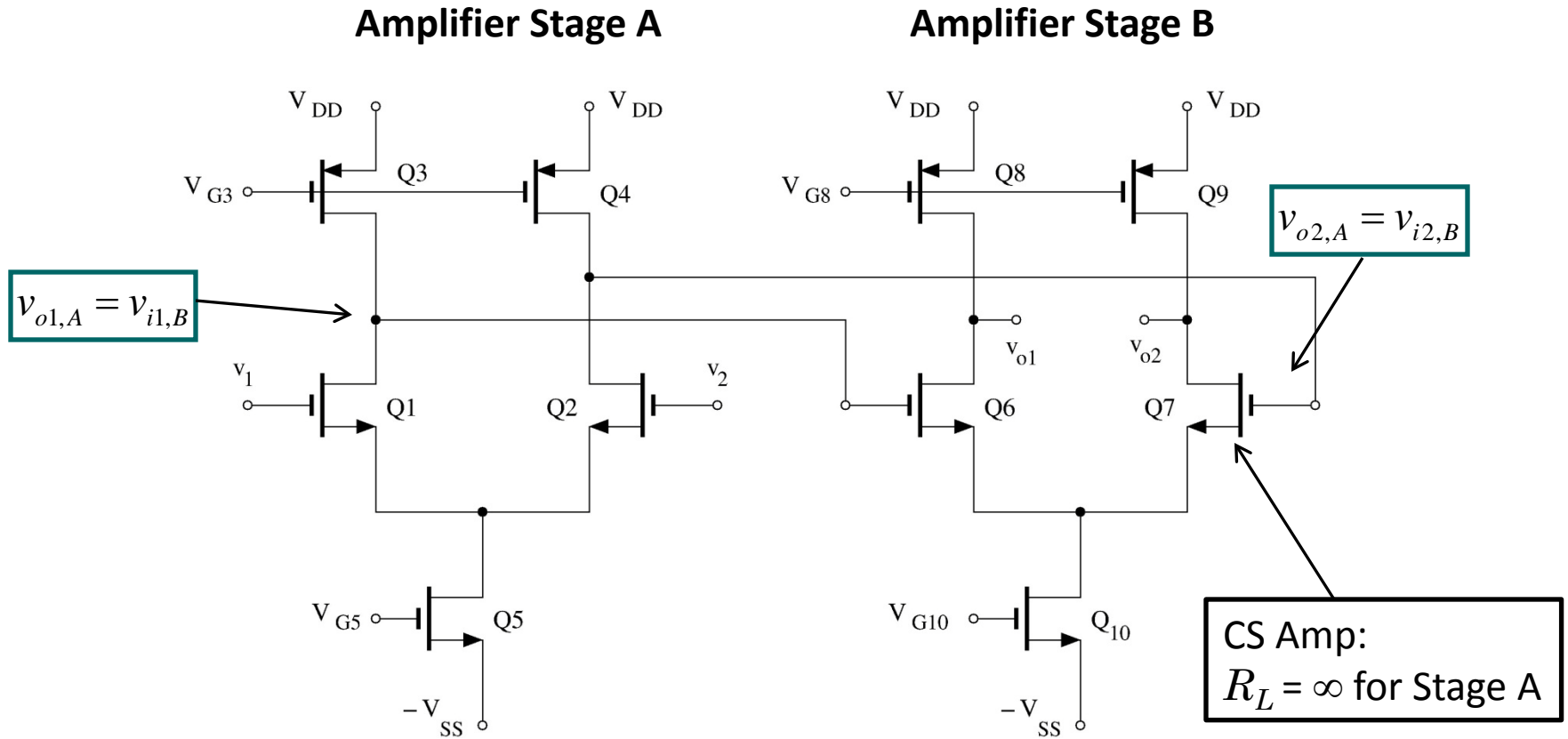Typical implementation of differential amplifiers with two outputs




Differential Amplifiers with Single-ended Output


Single-ended Output

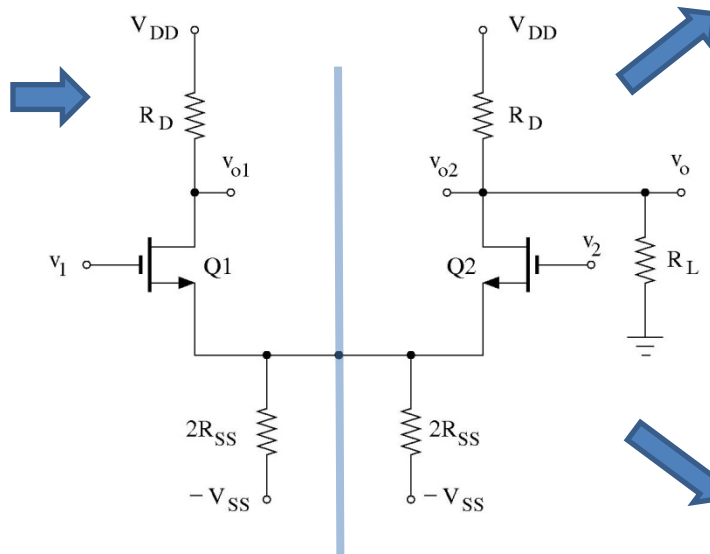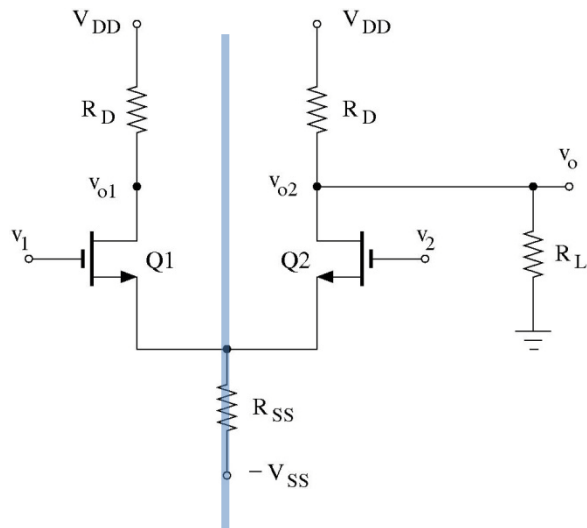

Differential Mode

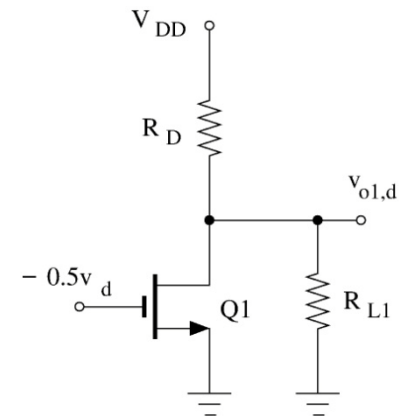

Common Mode

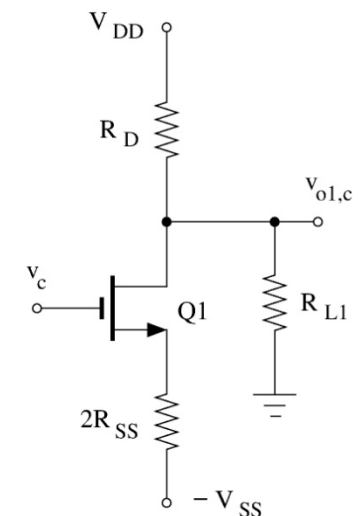


To use half circuit, R_L should be large enough such that symmetry is preserved (i.e. $R_L \gg R_o = R_D || r_o$)

Differential Amplifiers with Single-ended Output


$$v_o = A_c \cdot v_c + A_d \cdot v_d$$

Single-ended Output

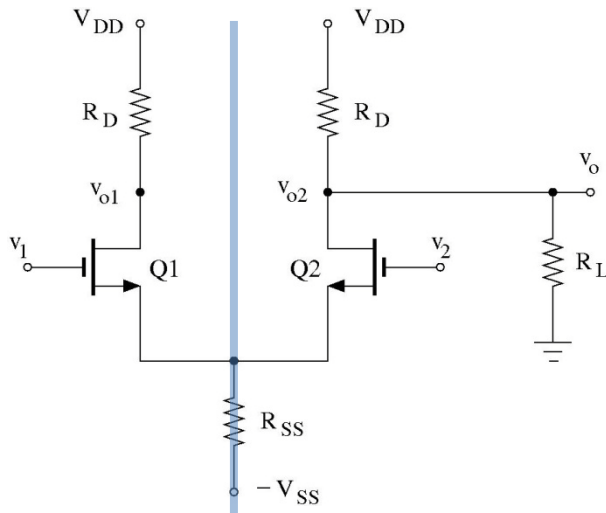

To use half circuit, R_L Should be large so that symmetry is preserved (i.e. $R_L \gg R_o = R_D || r_o$)

Differential Mode

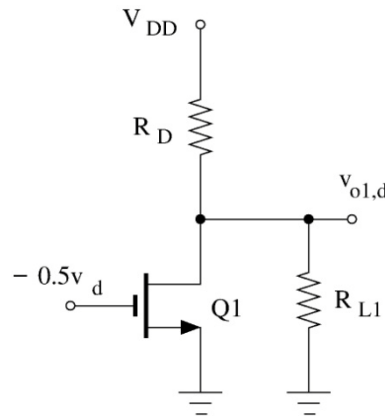


$$\frac{v_{o2}}{0.5v_d} = -g_m(r_o || R_D || R_L)$$

$$v_{od} = v_{o2} = -0.5g_m(r_o || R_D || R_L)v_d$$

$$A_d = \frac{v_{od}}{v_d} = -0.5g_m(r_o || R_D || R_L)$$

Common Mode

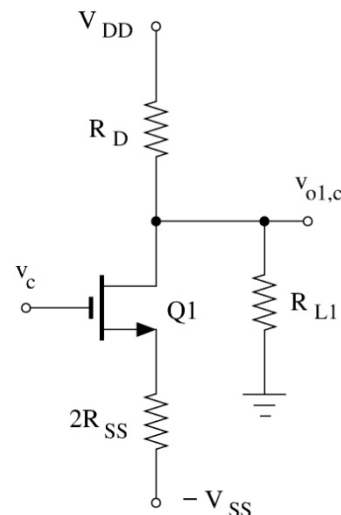


$$A_c = \frac{v_{oc}}{v_c} = -\frac{g_m(R_D || R_L)}{1 + 2g_m R_{SS} + (R_D || R_L)/r_o}$$

Note: $A_c \neq 0$ which means CMMR is NOT infinite.


An implementation of differential amplifiers with an output (coupled to a CS amplifier)

Differential Amplifier with a single output


CS stage

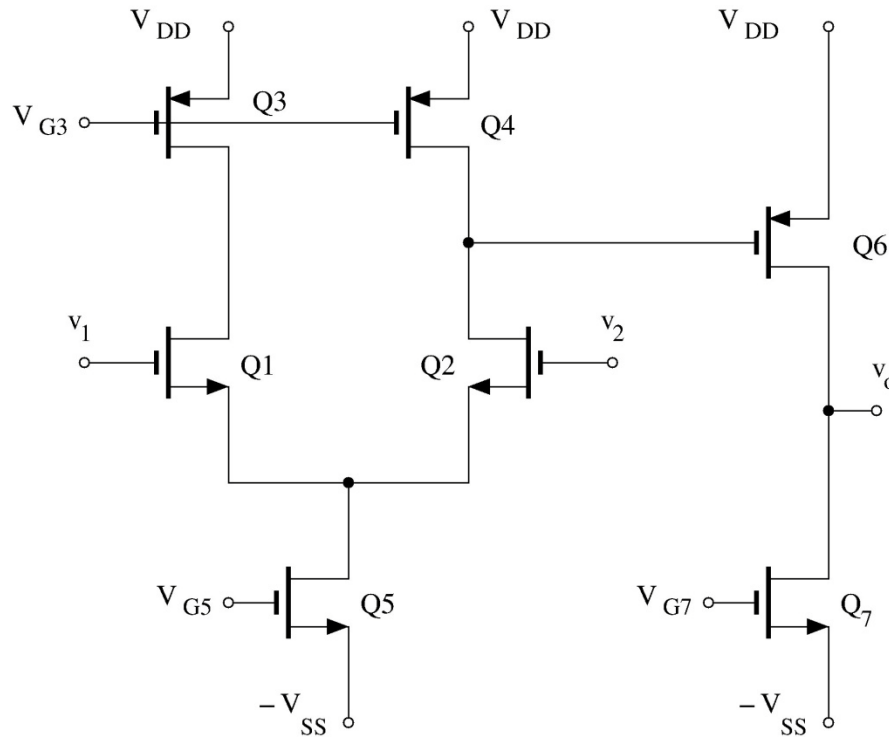

Active load for a single-ended output

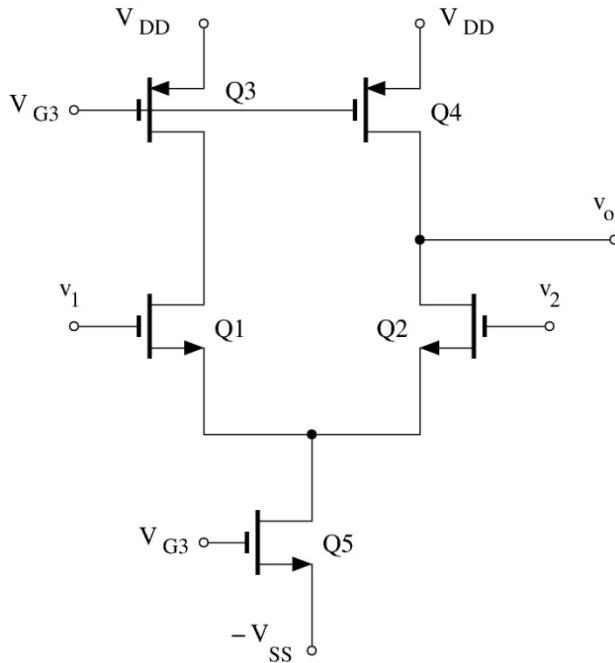

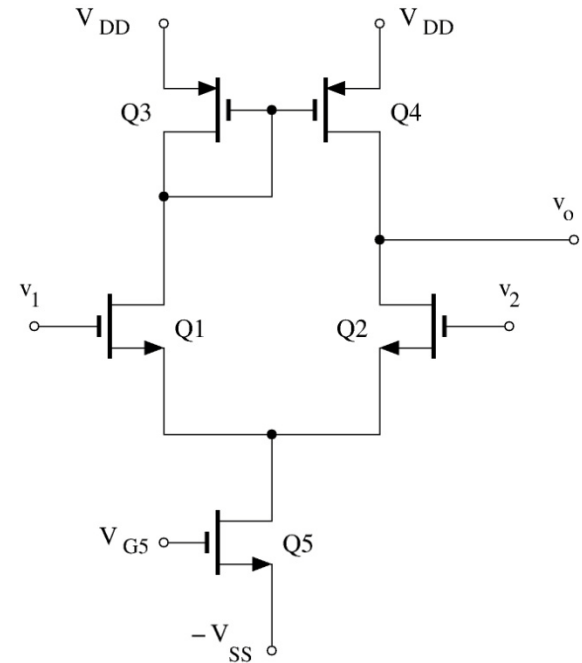
Works fine but require biasing of Q3 and Q4 (i.e., V_{G3})




“Popular” active load for single-ended output

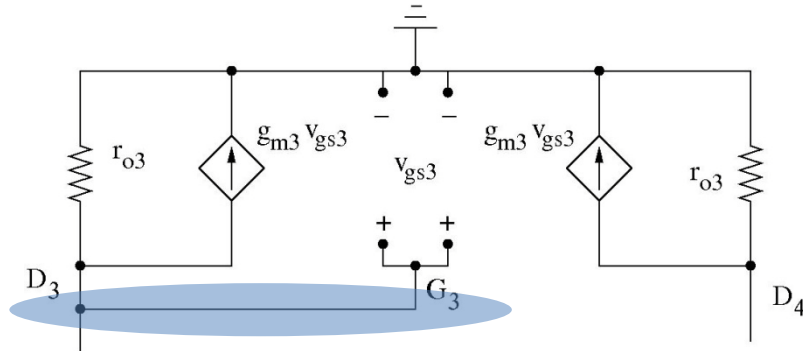- Q3/Q4 are NOT current sources and do not require biasing (i.e., V_{G3})
- Gets a similar gain and CMRR
- But, circuit is NOT symmetric (half-circuit does not work!)


Active load for a single-ended output: Small signal equivalent





Small Signal

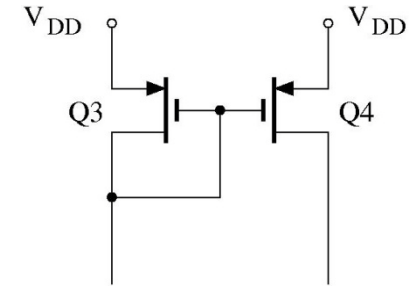

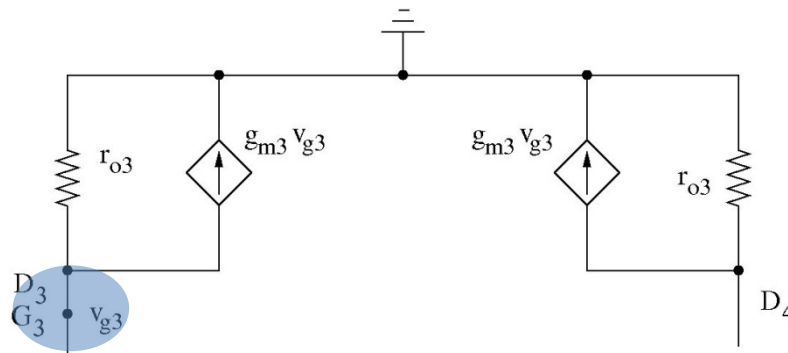
Note $r_{o4} = r_{o3}$ and $g_{m4} = g_{m3}$



Diode-connected
transistor

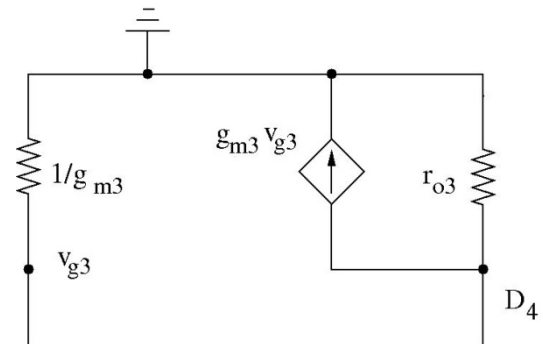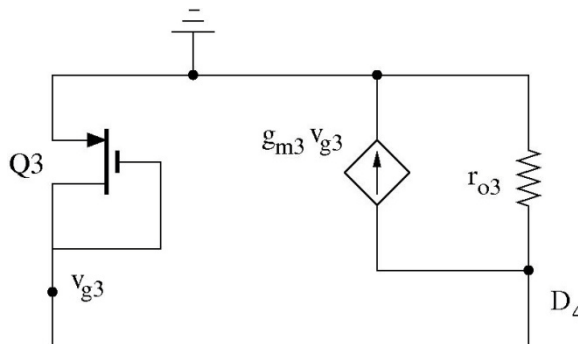

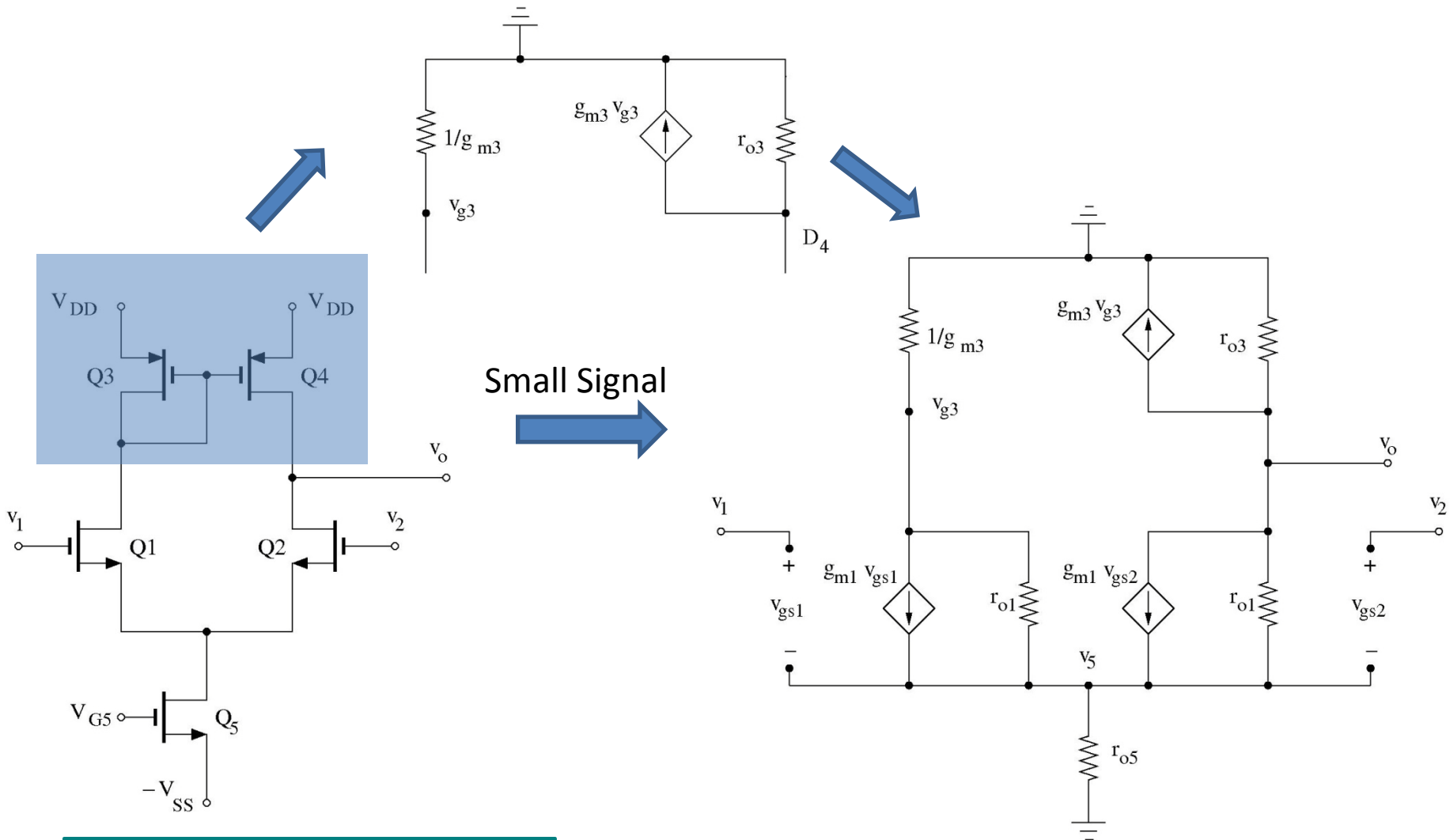
Small-signal analysis of single-ended output



Note $r_{o4} = r_{o3}$ and $g_{m4} = g_{m3}$
 $r_{o2} = r_{o1}$ and $g_{m2} = g_{m1}$

**Circuit is NOT symmetric
 CANNOT use "half-circuit"**

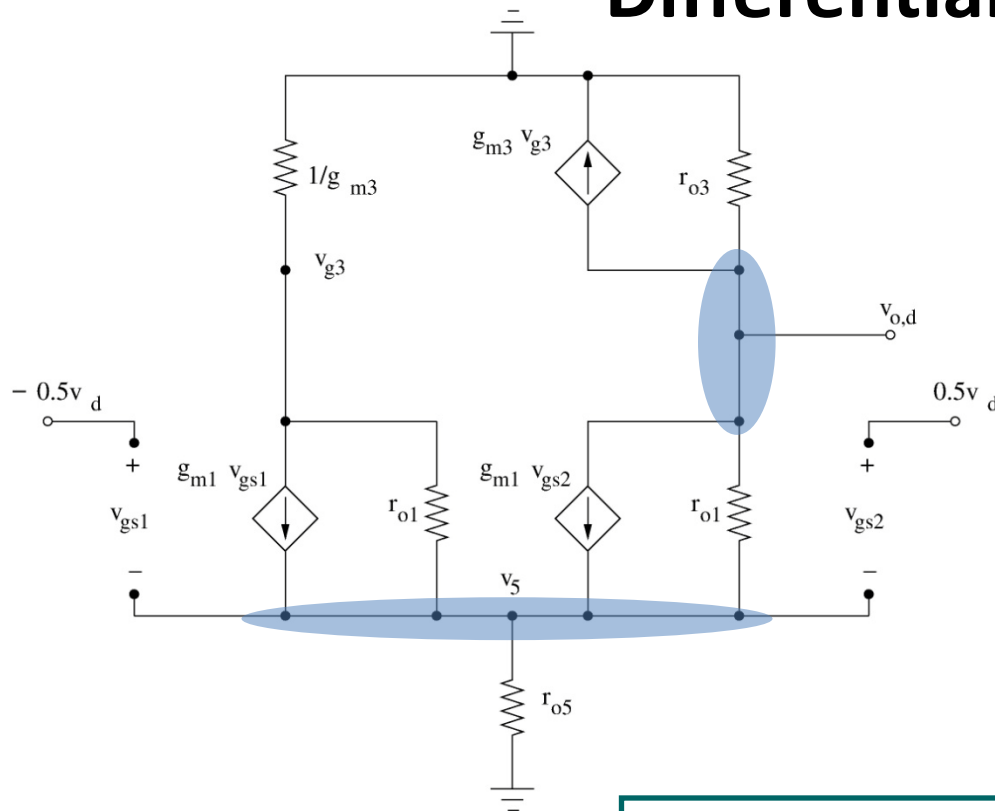Small-signal analysis of single-ended output – Differential Gain (1)



$$\begin{aligned} r_{o4} &= r_{o3} \text{ and } g_{m4} = g_{m3} \\ r_{o2} &= r_{o1} \text{ and } g_{m2} = g_{m1} \\ v_{gs1} &= -0.5v_d - v_5 \\ v_{gs2} &= +0.5v_d - v_5 \end{aligned}$$

Node v_{g3}

$$g_{m3}v_{g3} + g_{m1}(-0.5v_d - v_5) + \frac{v_{g3} - v_5}{r_{o1}} = 0$$

Node v_o

$$g_{m3}v_{g3} + \frac{v_o}{r_{o3}} + g_{m1}(+0.5v_d - v_5) + \frac{v_o - v_5}{r_{o1}} = 0$$

Node v_5

$$\frac{v_5}{r_{o5}} + \frac{v_5 - v_{g3}}{r_{o1}} + \frac{v_5 - v_o}{r_{o1}} - g_{m1}(-0.5v_d - v_5) - g_{m1}(+0.5v_d - v_5) = 0$$

Small-signal analysis of single-ended output – Differential Gain (2)

Rearranging terms:

$$v_{g3} \left(g_{m3} + \frac{1}{r_{o1}} \right) + v_5 \left(-g_{m1} - \frac{1}{r_{o1}} \right) = +0.5 g_{m1} v_d$$

$$v_{g3} (g_{m3}) + v_5 \left(-g_{m1} - \frac{1}{r_{o1}} \right) + v_o \left(\frac{1}{r_{o3}} + \frac{1}{r_{o1}} \right) = -0.5 g_{m1} v_d$$


$$v_{g3} \left(-\frac{1}{r_{o1}} \right) + v_5 \left(+2g_{m1} + \frac{2}{r_{o1}} + \frac{1}{r_{o5}} \right) + v_o \left(-\frac{1}{r_{o1}} \right) = 0$$

Dropping $1/r_o$ terms compared with g_m

$$v_{g3} (g_{m3}) + v_5 (-g_{m1}) = +0.5 g_{m1} v_d$$

$$v_{g3} (g_{m3}) + v_5 (-g_{m1}) + v_o \left(\frac{1}{r_{o3}} + \frac{1}{r_{o1}} \right) = -0.5 g_{m1} v_d$$
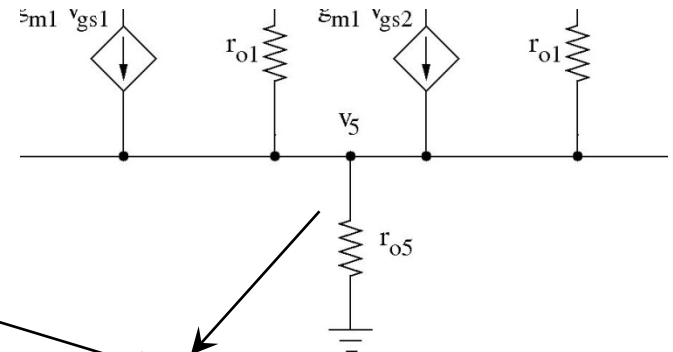
$$v_{g3} \left(-\frac{1}{r_{o1}} \right) + v_5 (+2g_{m1}) + v_o \left(-\frac{1}{r_{o1}} \right) = 0$$



Dropping v_5/r_{o5} term implies that very little current flows into r_{o5} (can remove r_{o5} from the circuit as done in the textbook)

Small-signal analysis of single-ended output – Differential Gain (3)

$$v_{g3}(g_{m3}) + v_5(-g_{m1}) = +0.5g_{m1}v_d$$

$$v_{g3}(g_{m3}) + v_5(-g_{m1}) + v_o\left(\frac{1}{r_{o3}} + \frac{1}{r_{o1}}\right) = -0.5g_{m1}v_d$$

$$v_{g3}\left(-\frac{1}{r_{o1}}\right) + v_5(+2g_{m1}) + v_o\left(-\frac{1}{r_{o1}}\right) = 0$$

Subtracting second equation from the first*:

$$\frac{v_o}{r_{o1} \parallel r_{o3}} = -g_{m1}v_d \Rightarrow v_o = -g_{m1}(r_{o1} \parallel r_{o3})v_d \Rightarrow A_d = -g_{m1}(r_{o1} \parallel r_{o3})$$

Adding all three equations give:

$$2g_{m3}v_{g3} + \frac{v_o}{r_{o3}} = 0 \Rightarrow v_{g3} = -\frac{v_o}{2g_{m3}r_{o3}}$$


Note: $v_{g3} \ll v_o$

$$v_{g3} = +\frac{g_{m1}(r_{o1} \parallel r_{o3})}{2g_{m3}r_{o3}}v_d \approx \frac{g_{m1}}{4g_{m3}r_o}v_d$$

Textbook Eq. 7.1.40 is incorrect

* This is sloppy math as if subtract 2nd equation from first before dropping r_o terms, a v_{g3} term appears in the above equation. Fortunately, as $v_{g3} \ll v_o$, ignoring v_{g3} term is justified

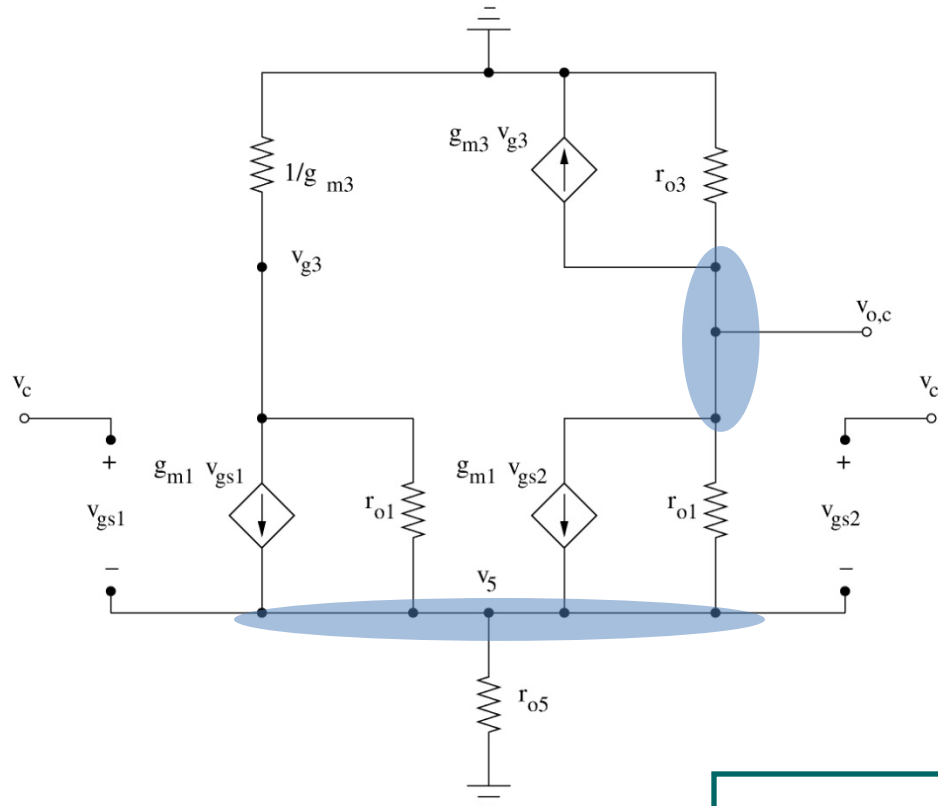Small-signal analysis of single-ended output – Common-mode Gain (1)



$$\begin{aligned} r_{o4} &= r_{o3} \text{ and } g_{m4} = g_{m3} \\ r_{o2} &= r_{o1} \text{ and } g_{m2} = g_{m1} \\ v_{gs1} &= -0.5v_d - v_5 \\ v_{gs2} &= +0.5v_d - v_5 \end{aligned}$$

Node v_{g3}

$$g_{m3}v_{g3} + g_{m1}(v_c - v_5) + \frac{v_{g3} - v_5}{r_{o1}} = 0$$

Node v_o

$$g_{m3}v_{g3} + \frac{v_o}{r_{o3}} + g_{m1}(v_c - v_5) + \frac{v_o - v_5}{r_{o1}} = 0$$

Node v_5

$$\frac{v_5}{r_{o5}} + \frac{v_5 - v_{g3}}{r_{o1}} + \frac{v_5 - v_o}{r_{o1}} - g_{m1}(v_c - v_5) - g_{m1}(v_c - v_5) = 0$$

Small-signal analysis of single-ended output – Common-mode Gain (2)

$$g_{m3}v_{g3} + g_{m1}(v_c - v_5) + \frac{v_{g3} - v_5}{r_{o1}} = 0$$

$$g_{m3}v_{g3} + \frac{v_o}{r_{o3}} + g_{m1}(v_c - v_5) + \frac{v_o - v_5}{r_{o1}} = 0$$

$$\frac{v_5}{r_{o5}} + \frac{v_5 - v_{g3}}{r_{o1}} + \frac{v_5 - v_o}{r_{o1}} - g_{m1}(v_c - v_5) - g_{m1}(v_c - v_5) = 0$$


Subtracting second equation from the first and dropping $1/r_o$ terms compared with g_m

$$\frac{v_o}{r_{o1} \parallel r_{o3}} = 0 \Rightarrow A_c = 0 \Rightarrow \text{CMRR} = \infty$$

Solving equations without dropping $1/r_o$ terms compared with g_m

$$v_o = \frac{1}{2g_{m3}r_{o5}}v_c \Rightarrow A_c = \frac{1}{2g_{m3}r_{o5}} \Rightarrow \text{CMRR} = 2g_{m3}r_{o5}g_{m1}(r_{o1} \parallel r_{o3})$$

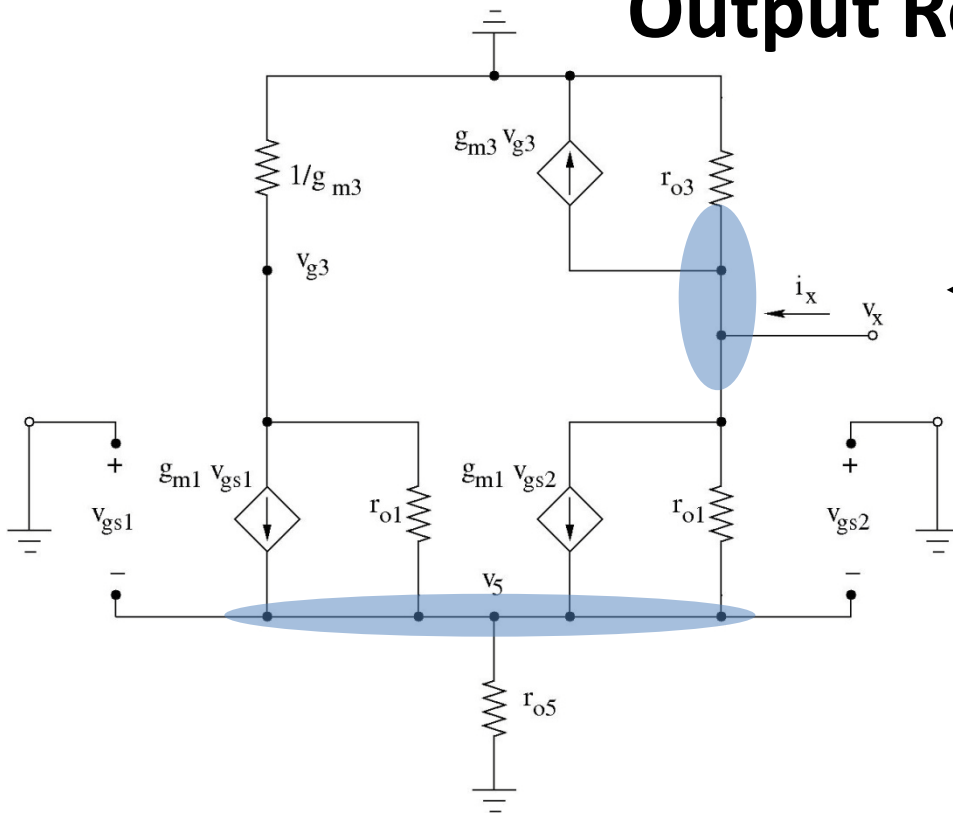Small-signal analysis of single-ended output – Output Resistance



Attach a source v_x to the output and calculate i_x)

$$\text{Node } v_{g3} \quad g_{m3}v_{g3} + g_{m1}(-v_5) + \frac{v_{g3} - v_5}{r_{o1}} = 0$$

$$\text{Node } v_x \quad g_{m3}v_{g3} + \frac{v_x}{r_{o3}} + g_{m1}(-v_5) + \frac{v_x - v_5}{r_{o1}} = i_x$$

$$\text{Node } v_5 \quad \frac{v_5}{r_{o5}} + \frac{v_5 - v_{g3}}{r_{o1}} + \frac{v_5 - v_x}{r_{o1}} - g_{m1}(-v_5) - g_{m1}(-v_5) = 0$$

Subtracting second equation from the first and dropping $1/r_o$ terms compared with g_m

$$\frac{v_x}{r_{o1} \parallel r_{o3}} = i_x$$

$$R_o = \frac{v_x}{i_x} = r_{o1} \parallel r_{o3}$$